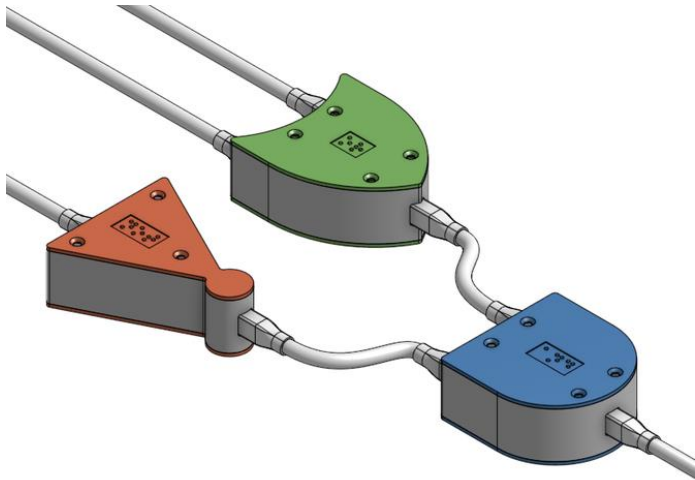




جامعة شقراء
Shaqra University



CS 211 - Digital Logic Design 211 عال - تصميم المنطق الرقمي

First Term - 1439/1440
Lecture #6

Dr. Hazem Ibrahim Shehata

Assistant Professor

College of Computing and Information Technology

Administrivia

➤ Assignment #1:

- Due: **Today**.
- Solution to be posted tomorrow.

➤ Midterm #1:

- Date: **Wednesday, October 24, 2018**.
- Time: 8:30am - 9:30am
- Scope: Chapters 2 and 3 (Lectures 1,2,3,4,5, and half-of-6).



Website: <http://hshehata.github.io/courses/su/cs211>



Chapter 3: Logic Gates (... Continuing ...)


Exclusive-OR (XOR) Gate

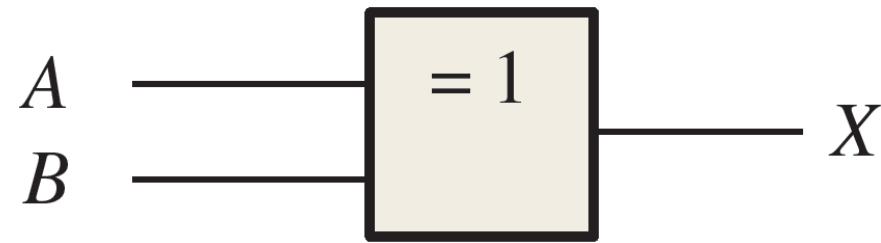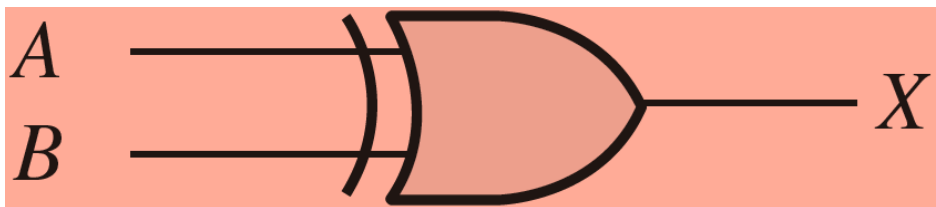- Performs operation called **modulo-2 addition**, which is the same as binary addition with no carry.
 - Takes 2^+ inputs, and produces 1 output.
 - Output is **High (1)** if and only if number of **High (1)** inputs is **odd**.
 - Output is **Low (0)** if and only if number of **High (1)** inputs is **even**.
- Symbols:



XOR Gate Truth Table


➤ For a 2-input XOR Gate:

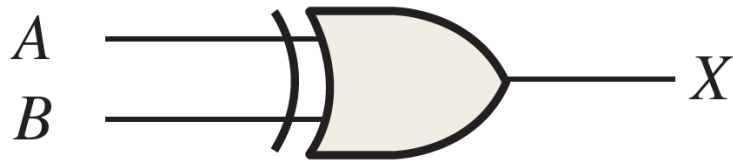

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

Example: Truth Table for 3-input XOR Gate


$$n = 3 \rightarrow N = 2^3 = 8$$

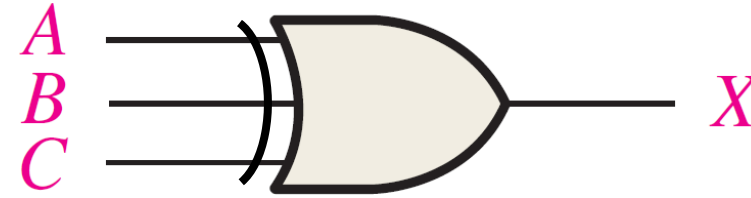

Inputs			Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>X</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Timing Diagram of XOR Gate


➤ **Example:** 2-input XOR Gate

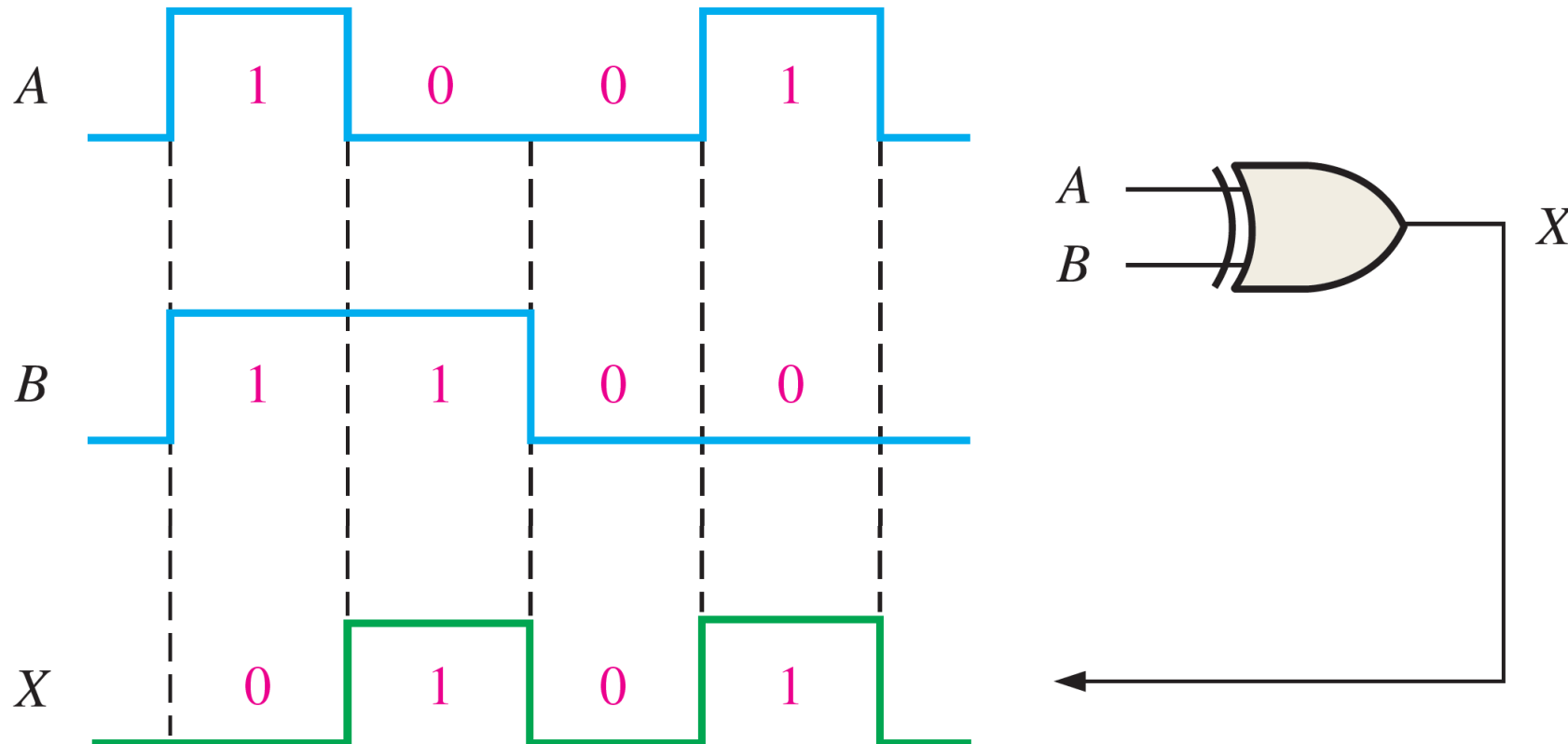

Application of XOR Gate

➤ **Example:** 1-bit Modulo-2 adder

Input Bits		Output (Sum)
<i>A</i>	<i>B</i>	Σ
0	0	0
0	1	1
1	0	1
1	1	0 (without the 1 carry bit)


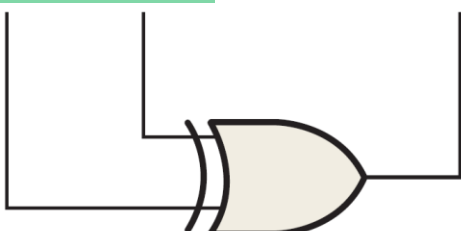


Exclusive-NOR (XNOR) Gate


➤ XOR with an inverted output.

- Takes 2+ inputs, and produces 1 output.
- Output is **Low (0)** if and only if number of **High (1)** inputs is **odd**.
- Output is **High (1)** if and only if number of **High (1)** inputs is **even**.

➤ Symbols:

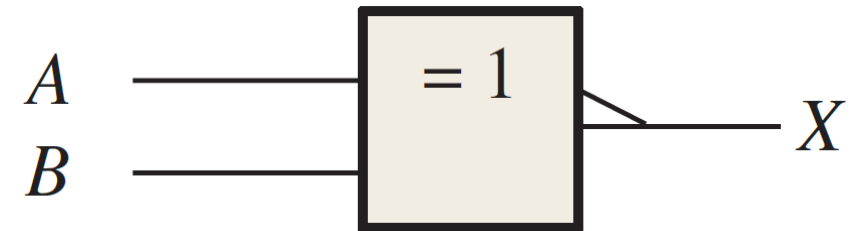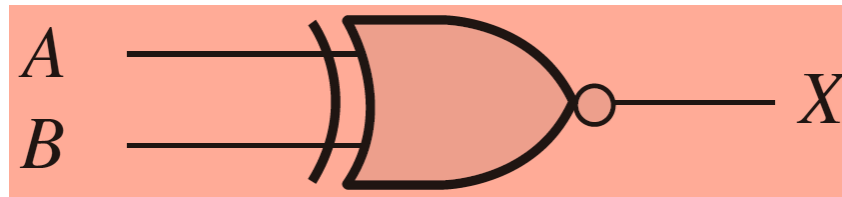


➤ Equivalent to:

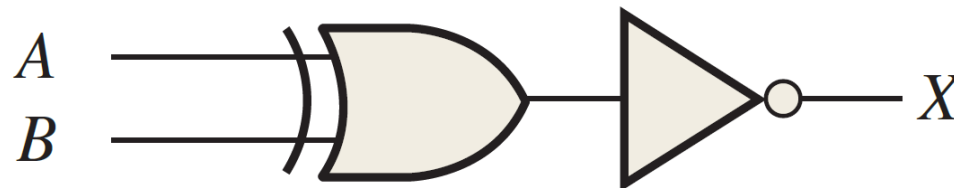

XNOR Gate Truth Table


➤ For a 2-input XNOR Gate:

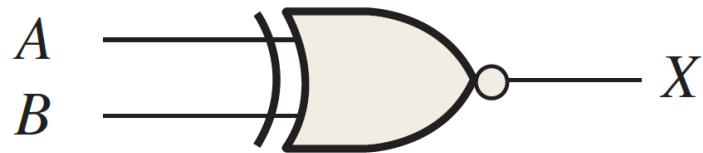

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	0
1	0	0
1	1	1

Example: Truth Table for 3-input XNOR Gate



$$n = 3 \rightarrow N = 2^3 = 8$$

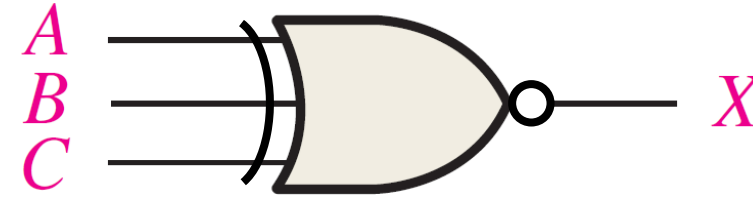

Inputs			Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>X</i>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


Timing Diagram of XNOR Gate

➤ **Example:** 2-input XNOR Gate

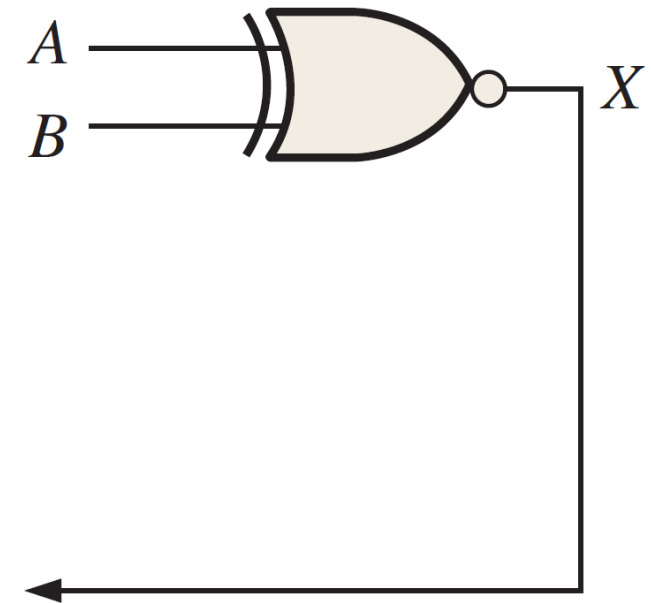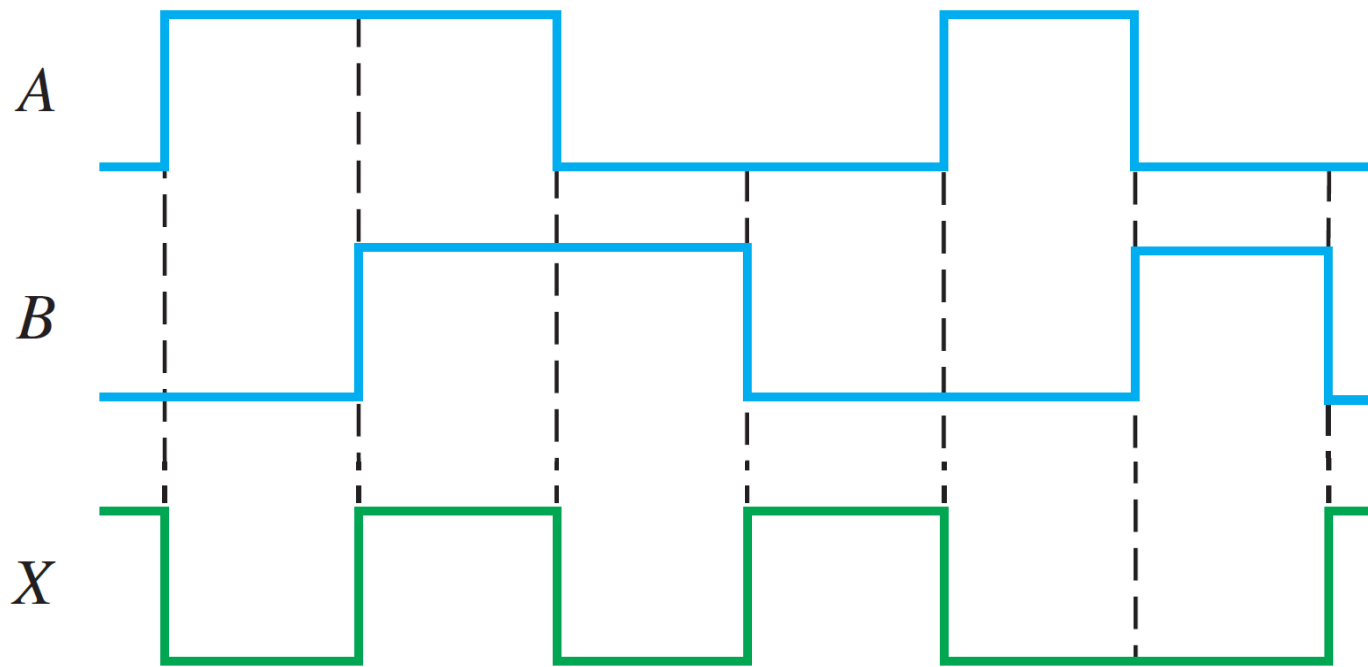

Application of XNOR Gate

➤ Example: 1-bit Binary Comparator

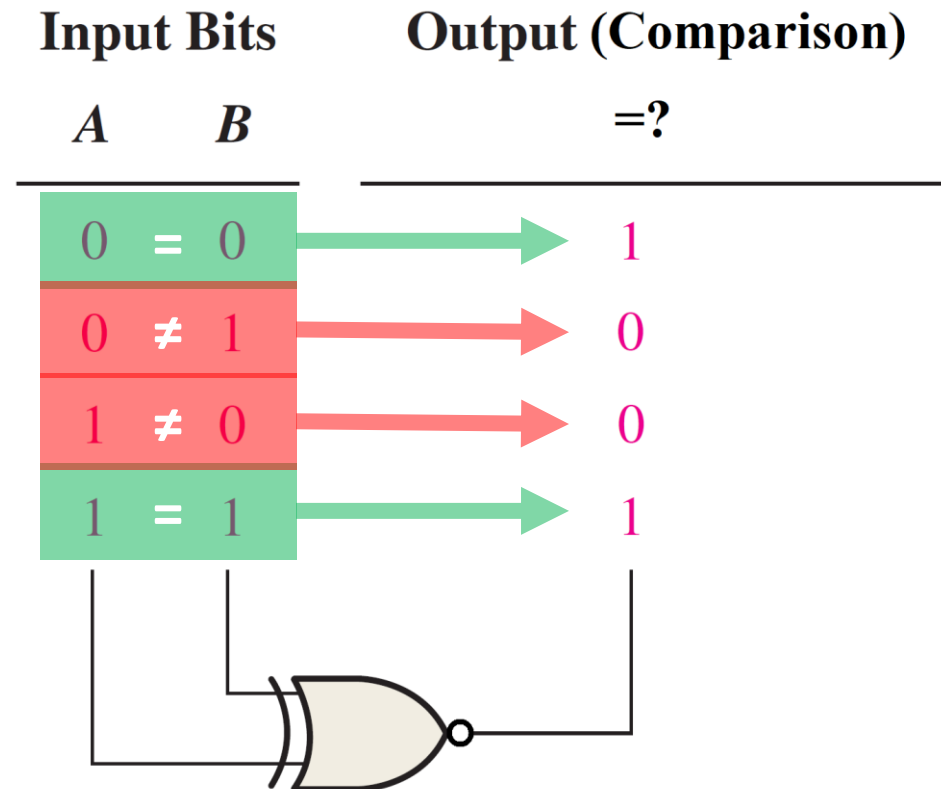




Chapter 4: Boolean Algebra and Logic Simplification

Basic Boolean Terms

- **Boolean Algebra (BA)**: the mathematics of digital logic.
- **Basic terms** in BA: Variable, Complement, Literal.
 1. **Variable**: symbol (usually an italic **uppercase letter** or word) to represent an action, a condition, or data. Any single variable can have only a 1 or a 0 value. **Example**: A or X .
 2. **Complement**: the inverse of a variable and is indicated by a bar over the variable (overbar). **Example**: \bar{A} or \bar{X} .
 3. **Literal**: variable or complement of a variable. **Example**: A or \bar{X} .

Boolean Addition

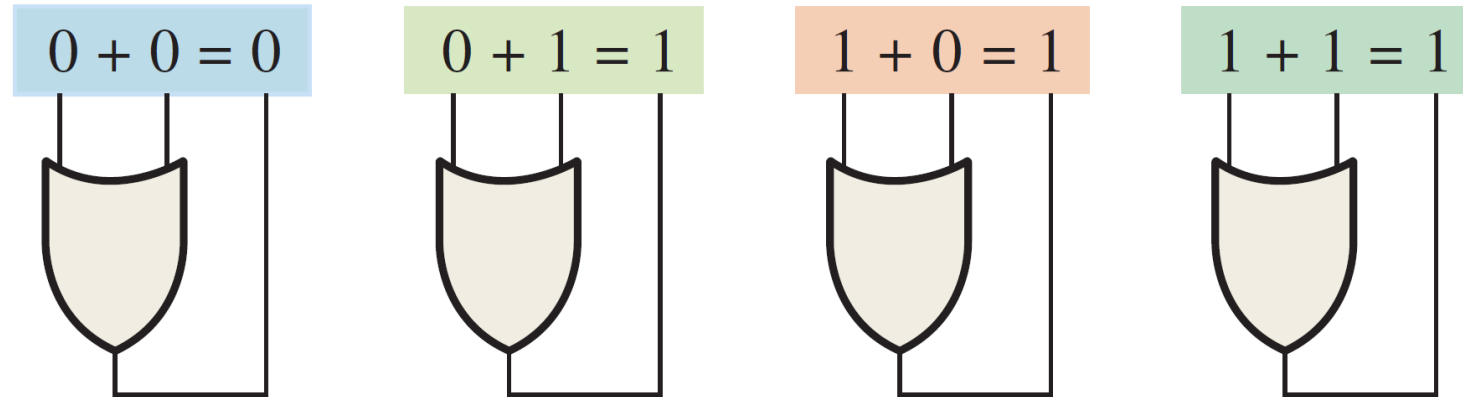➤ **Boolean addition** (+) is equivalent to **OR operation**.




➤ **Sum term**: sum of literals.

- Produced in logic circuits by **OR** operation with no AND's involved.
- Equals **1** if **1+** literals equals **1**. Equals **0** if **all** literals equal **0**.
- **Examples**: $A + \bar{B}$, $\bar{A} + B + C + \bar{D}$

Boolean Multiplication

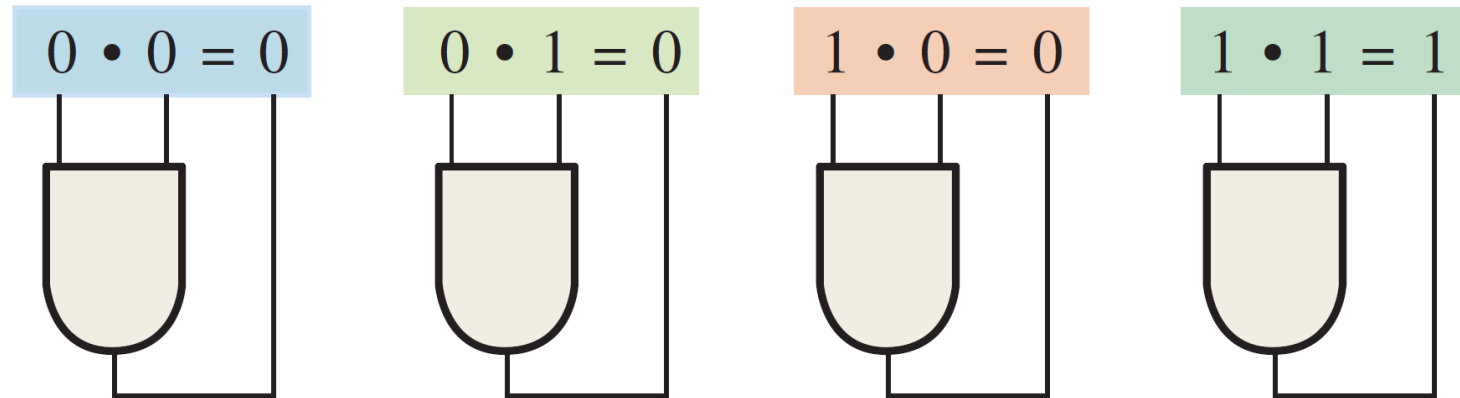➤ **Boolean multiplication** (\cdot) is equivalent to **AND operation**.



➤ **Product term**: product of literals.


- Produced in logic circuits by **AND** operation with no OR's involved.
- Equals **1** if **all** literals equal **1**. Equals **0** if **1+** literals equals **0**.
- **Examples**: $\bar{A} \cdot \bar{B}$, $A\bar{B}\bar{C}D$

Laws and Rules of Boolean Algebra


- Commutative Laws ($+$, \cdot)
- Associative Laws ($+$, \cdot)
- Distributive Law
- Rules of Boolean Algebra (12 rules)

Commutative Laws

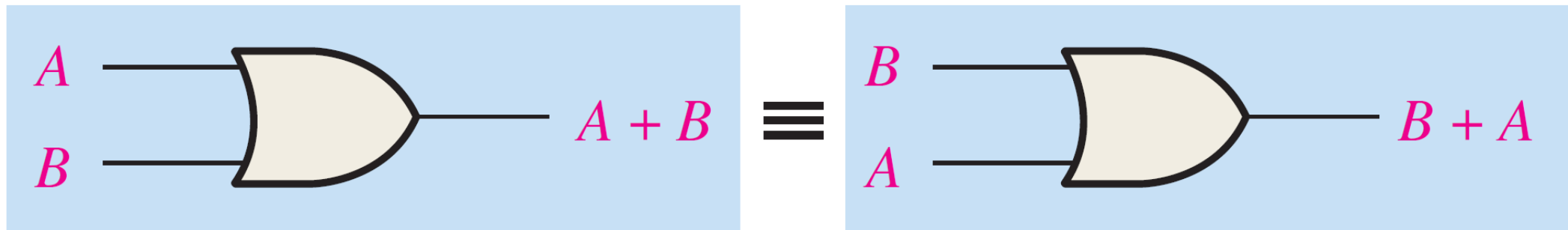➤ Commutative law of addition: $A + B = B + A$




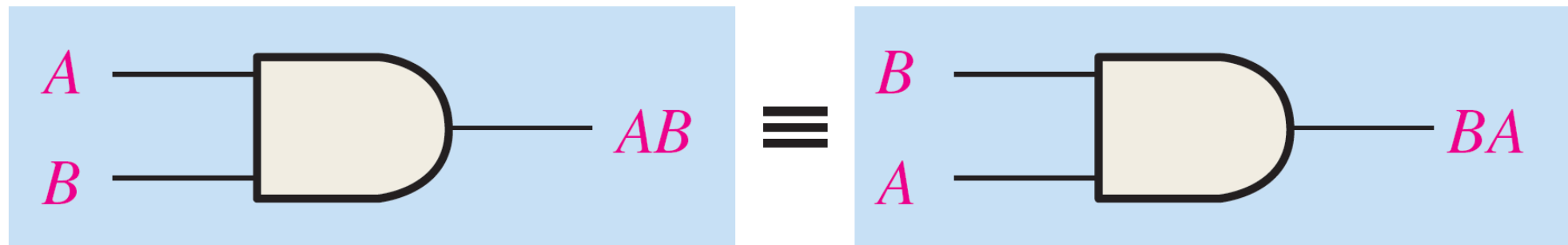➤ Commutative law of multiplication: $AB = BA$




Associative Laws

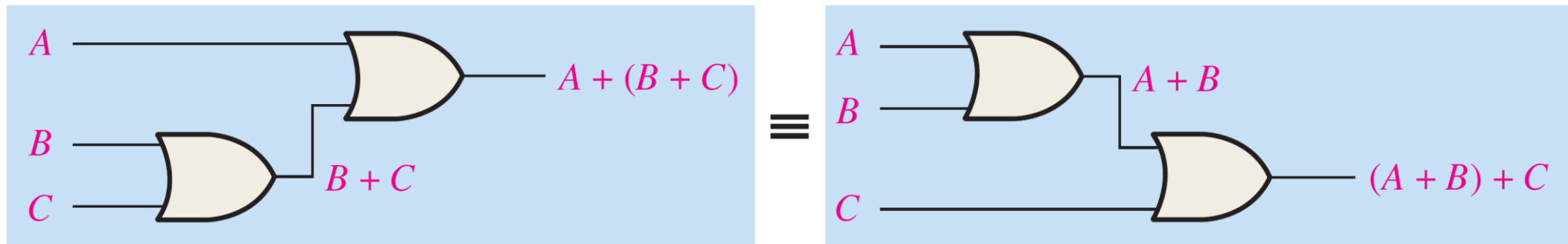➤ Associative law of addition: $A + (B + C) = (A + B) + C$




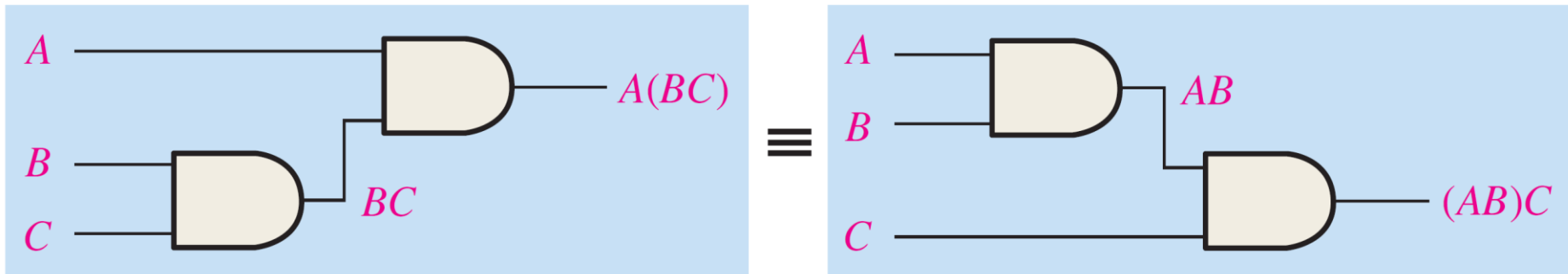➤ Associative law of multiplication: $A(BC) = (AB)C$




Distributive Law

➤ Distributive Law: $A(B + C) = AB + AC$

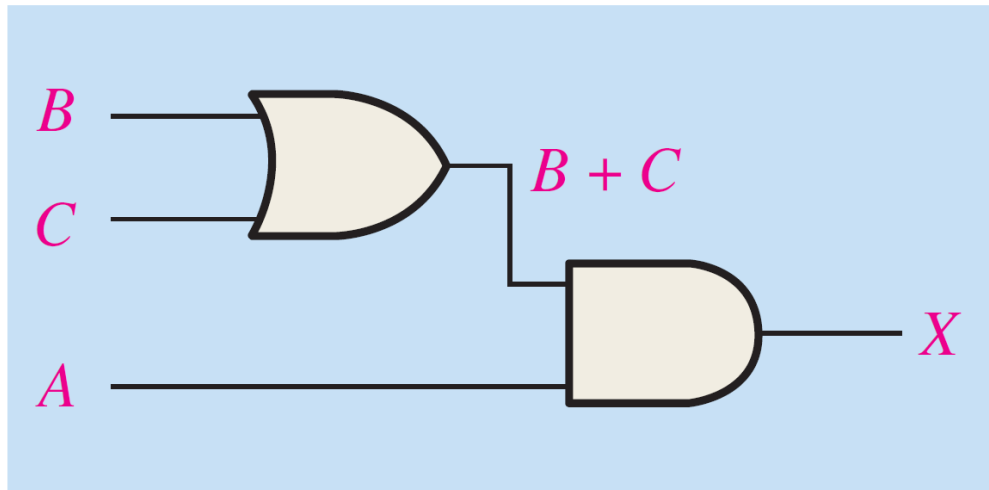

$$X = A(B + C)$$

\equiv

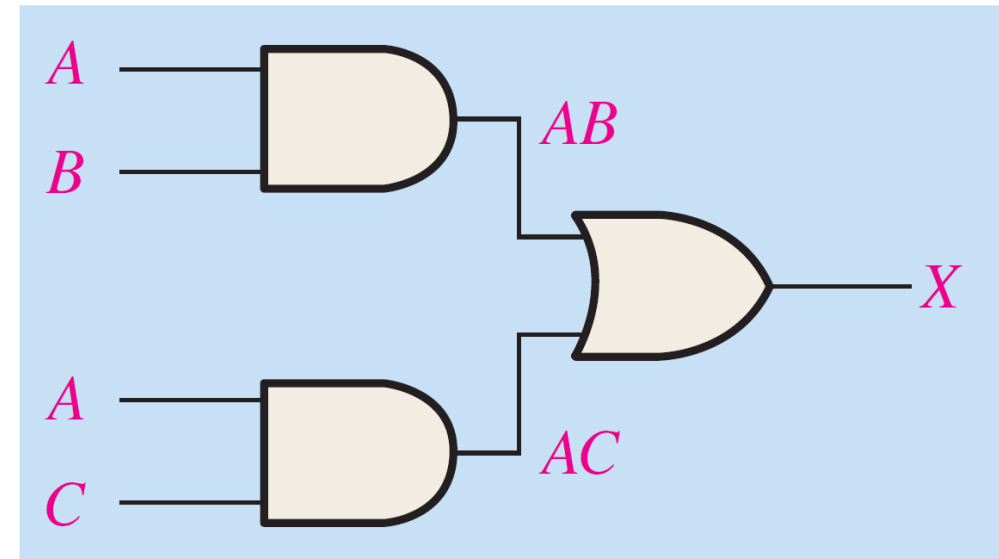


$$X = AB + AC$$

Rules of Boolean Algebra

➤ Rule 1: $A + 0 = A$




➤ Rule 2: $A + 1 = 1$

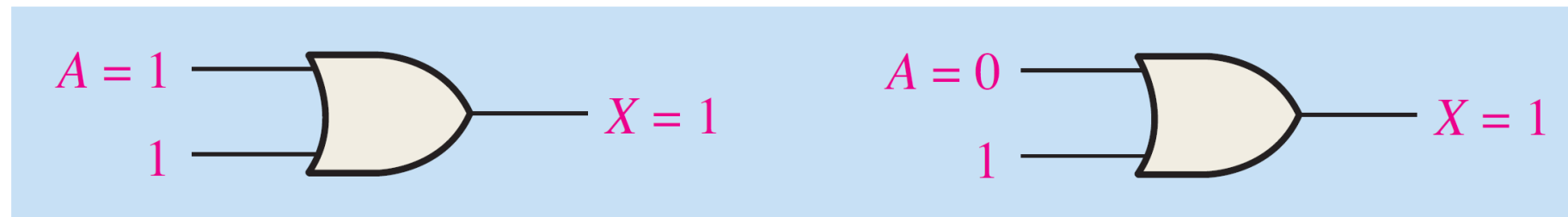

Rules of Boolean Algebra

➤ Rule 3: $A \cdot 0 = 0$

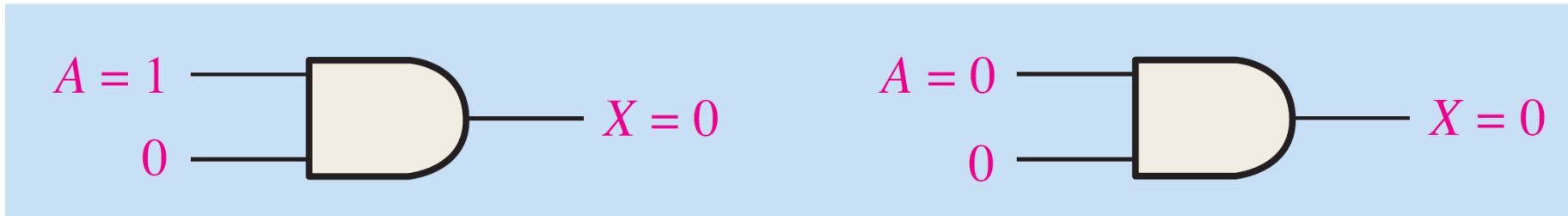


➤ Rule 4: $A \cdot 1 = A$



Rules of Boolean Algebra

➤ Rule 5: $A + A = A$


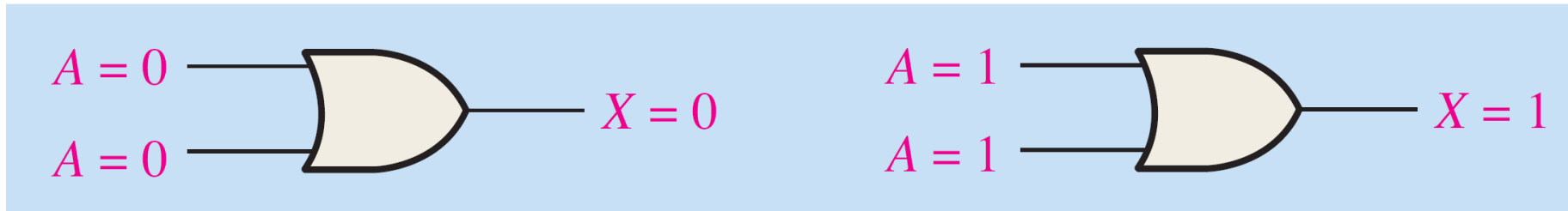


➤ Rule 6: $A + \bar{A} = 1$





Rules of Boolean Algebra

➤ Rule 7: $A \cdot A = A$

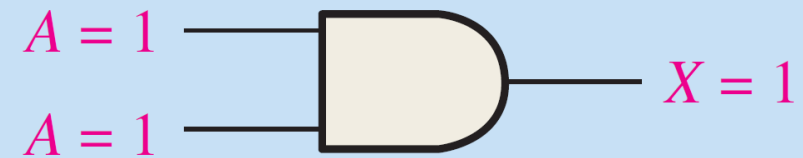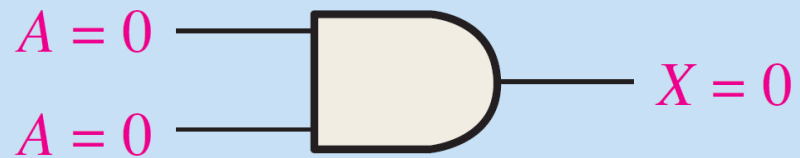


➤ Rule 8: $A \cdot \bar{A} = 0$

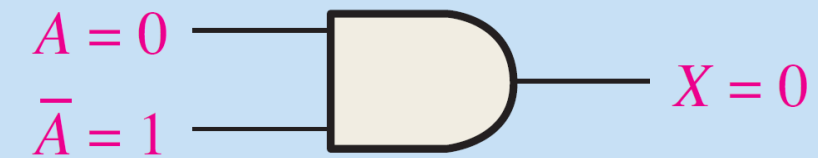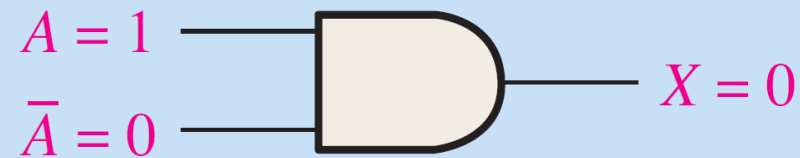

Rules of Boolean Algebra

➤ Rule 9: $\overline{\overline{A}} = A$

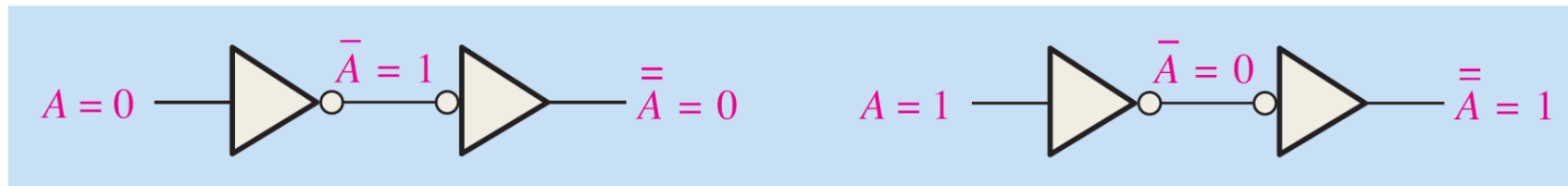

➤ Rule 10: $A + AB = A$

◦ Proof:

- L.H.S. = $A \cdot 1 + AB$ [R4]
- = $A(1 + B)$ [Dist. Law]
- = $A \cdot 1$ [R2]
- = A [R4]
- = R.H.S.

A	B	AB	$A + AB$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

↑ equal ↑


Rules of Boolean Algebra

➤ Rule 11: $A + \bar{A}B = A + B$

◦ Proof:

- L.H.S. = $A + AB + \bar{A}B$ [R10] = $A + (A + \bar{A})B$ [Dist. Law]
- = $A + 1 \cdot B$ [R6] = $A + B$ [R4] = R.H.S.

A	B	$\bar{A}B$	$A + \bar{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

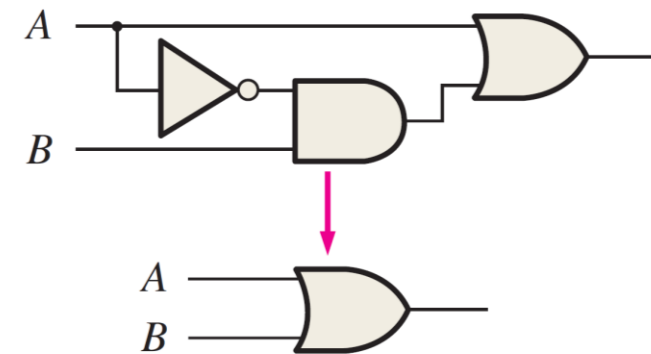

Rules of Boolean Algebra

➤ **Rule 12:** $(A + B)(A + C) = A + BC$

◦ **Proof:**

- L.H.S. = $AA + AC + AB + BC$ [Dist. Law]
- $= A + AC + AB + BC$ [R7]
- $= A(1 + C) + AB + BC$ [Dist. Law]
- $= A \cdot 1 + AB + BC$ [R2]
- $= A + AB + BC$ [R4]
- $= A(1 + B) + BC$ [Dist. Law]
- $= A \cdot 1 + BC$ [R2]
- $= A + BC$ [R4]
- $= \text{R.H.S.}$

Rules of Boolean Algebra

➤ **Rule 12:** $(A + B)(A + C) = A + BC$ (...Continuing...)

◦ **Proof:**

A	B	C	$A + B$	$A + C$	$(A + B)(A + C)$	BC	$A + BC$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

Rules of Boolean Algebra - Summary

Basic rules of Boolean algebra.

1. $A + 0 = A$

2. $A + 1 = 1$

3. $A \cdot 0 = 0$

4. $A \cdot 1 = A$

5. $A + A = A$

6. $A + \bar{A} = 1$

7. $A \cdot A = A$

8. $A \cdot \bar{A} = 0$

9. $\bar{\bar{A}} = A$

10. $A + AB = A$

11. $A + \bar{A}B = A + B$

12. $(A + B)(A + C) = A + BC$

A , B , or C can represent a single variable or a combination of variables.

Reading Material

- Floyd, Chapter 3:
 - Pages 130 - 134
- Floyd, Chapter 4:
 - Pages 172 - 179