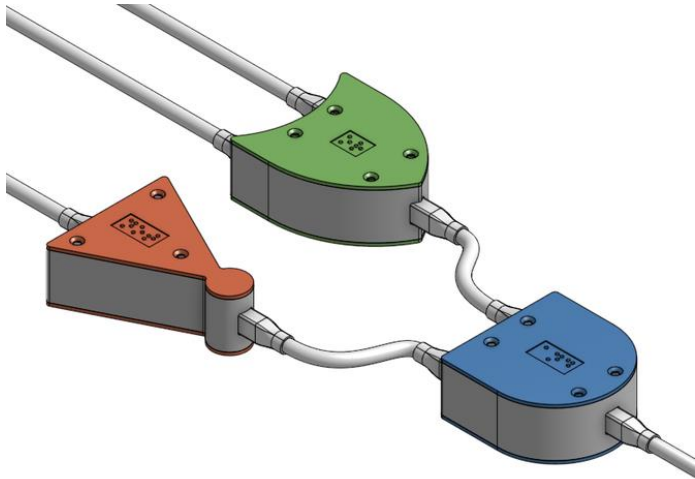




جامعة شقراء
Shaqla University



CS 211 - Digital Logic Design 211 عال - تصميم المنطق الرقمي

First Term - 1439/1440
Lecture #7

Dr. Hazem Ibrahim Shehata

Assistant Professor

College of Computing and Information Technology

Administrivia

➤ Midterm #1:

- Date: **Wednesday, October 24, 2018.**
- Time: 8:30am - 9:30am
- Scope: Chapters 2 and 3 (Lectures 1, 2, 3, 4, 5, and first part of 6).

➤ Tutorial:

- There will be no tutorial this Sunday!
- Instead, there will be a review tutorial on Monday at 12:30pm.

Website: <http://hshehata.github.io/courses/su/cs211>



Chapter 4: Boolean Algebra ... (... Continuing ...)

Laws and Rules of Boolean Algebra

➤ Five Laws

- **CL1:** $A + B = B + A$
- **CL2:** $AB = BA$
- **AL1:** $A + (B + C) = (A + B) + C$
- **AL2:** $A(BC) = (AB)C$
- **DL:** $A(B + C) = AB + AC$

➤ Twelve Rules


- **R1:** $A + 0 = A$
- **R2:** $A + 1 = 1$
- **R3:** $A \cdot 0 = 0$
- **R4:** $A \cdot 1 = A$
- **R5:** $A + A = A$
- **R6:** $A + \bar{A} = 1$
- **R7:** $A \cdot A = A$
- **R8:** $A \cdot \bar{A} = 0$
- **R9:** $\bar{\bar{A}} = A$
- **R10:** $A + AB = A$
- **R11:** $A + \bar{A}B = A + B$
- **R12:** $(A + B)(A + C) = A + BC$

DeMorgan's Theorems

➤ DeMorgan's First Theorem:

- States that: “The **complement** of a **product** of variables is equal to the **sum** of the **complements** of the variables”.
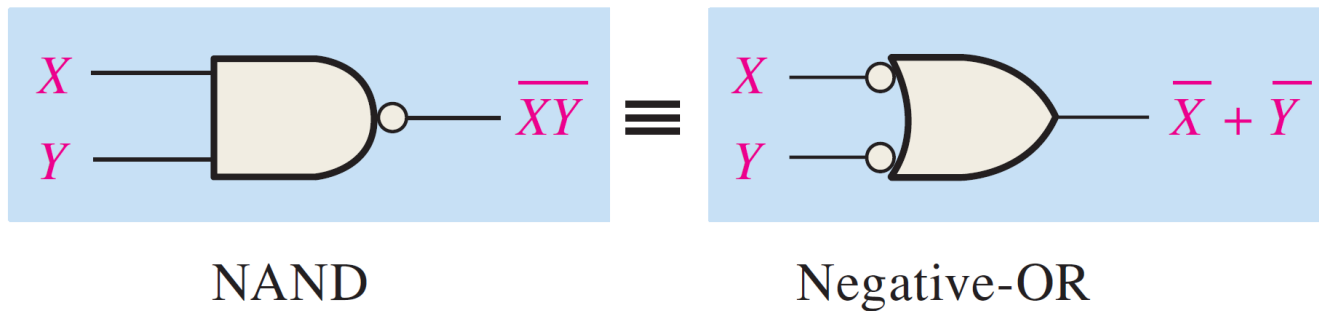
$$\overline{XY} = \overline{X} + \overline{Y}$$




Inputs		Output	
X	Y	\overline{XY}	$\overline{X} + \overline{Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

DeMorgan's Theorems (DMT)

➤ DeMorgan's Second Theorem:

- States that: “The **complement** of a **sum** of variables is equal to the **product** of the **complements** of the variables”.
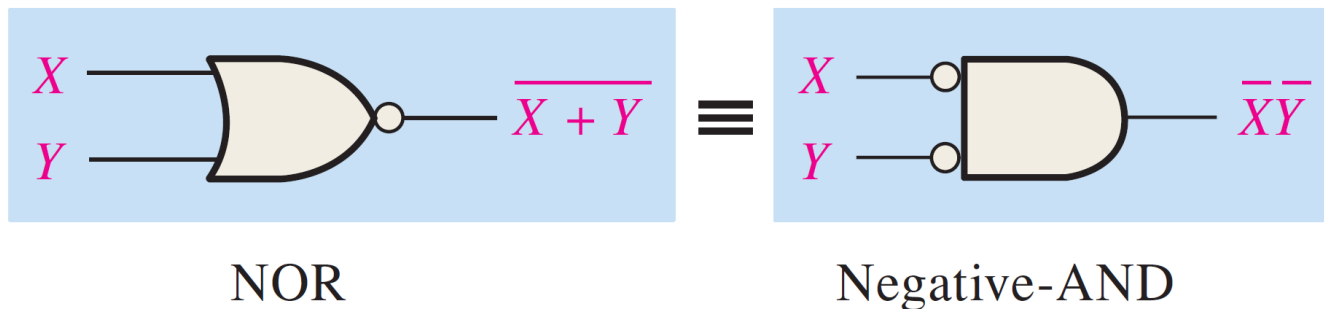
$$\overline{X + Y} = \overline{X} \overline{Y}$$



Inputs		Output	
X	Y	$\overline{X + Y}$	$\overline{X} \overline{Y}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

Applying DeMorgan's Theorems

➤ **Example:** Apply DeMorgan's theorems to the expressions:
 \overline{WXYZ} and $\overline{W + X + Y + Z}$.

➤ **Solution:**

- $\overline{WXYZ} = \bar{W} + \bar{X} + \bar{Y} + \bar{Z}$
- $\overline{W + X + Y + Z} = \bar{W}\bar{X}\bar{Y}\bar{Z}$

Applying DeMorgan's Theorems

➤ **Example:** Develop Boolean expression for XNOR gate given that Boolean expression for XOR gate is: $A\bar{B} + \bar{A}B$.

➤ **Solution:**

- XNOR Output = $\overline{A\bar{B} + \bar{A}B}$
- $= (\overline{A\bar{B}})(\overline{\bar{A}B})$ [DeMorgan's Theorem]
- $= (\bar{A} + \bar{\bar{B}})(\bar{\bar{A}} + \bar{B})$ [DeMorgan's Theorem]
- $= (\bar{A} + B)(A + \bar{B})$ [Rule 9]
- $= \bar{A}A + \bar{A}\bar{B} + AB + B\bar{B}$ [Distributive Law]
- $= \bar{A}\bar{B} + AB$ [Rule 8]

Boolean Analysis of Logic Circuits

➤ **Goal:** Given a logic circuit, can we construct a truth table for its output?!

➤ **Method:**


1. **Derive** Boolean expression for the logic circuit (i.e., output).
2. **Evaluate** Boolean expression (know what inputs make it 1).
3. **Put** evaluation results in a truth table format.

Boolean Analysis of Logic Circuits

1. Derive Boolean Expression for Logic Circuit

- Begin at left-most inputs and work toward final output, writing expression for each gate.

➤ Example:

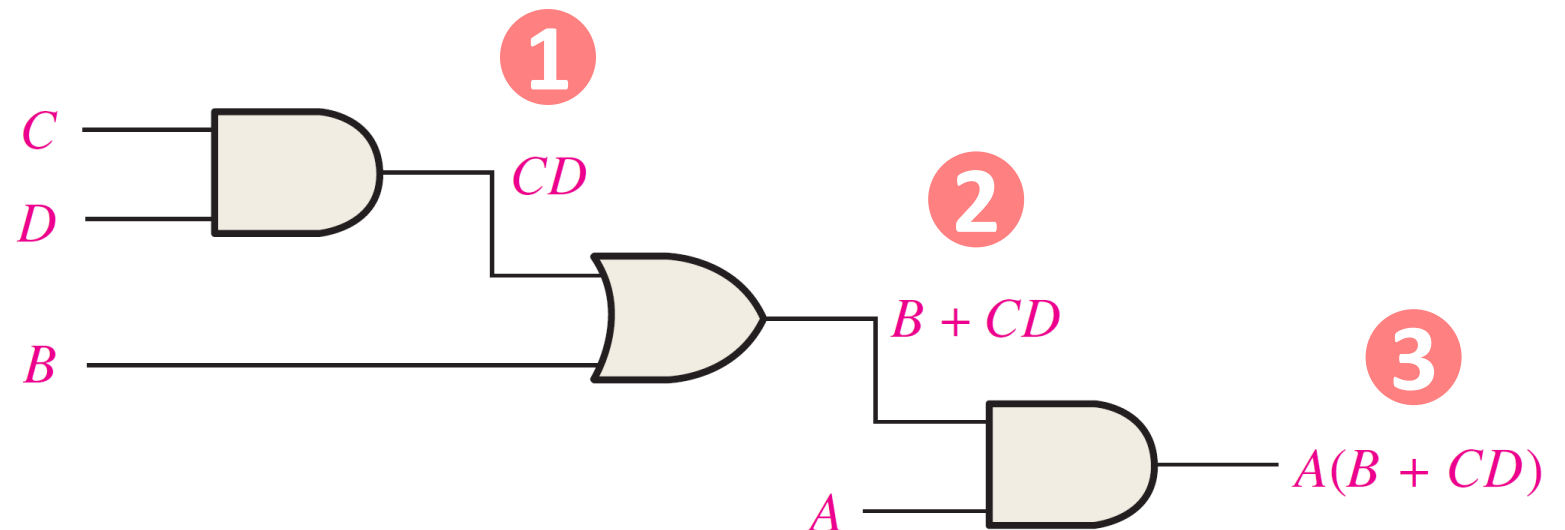

Boolean Analysis of Logic Circuits

2. Evaluate Expression

- Find the values of the variables that make the expression equal to 1!

➤ Example:

- Expression = $A(B + CD)$

To make $A(B + CD) = 1$:

➔ $A = 1$ and $B + CD = 1$

➔ $A = 1$ and
 $(B = 1$ or $CD = 1)$

➔ $A = 1$ and
 $(B = 1$ or $(C = 1$ and $D = 1))$

➔ $A = B = 1$ or $A = C = D = 1$

Boolean Analysis of Logic Circuits

3. Put Results in Truth Table Format

- Place a 1 in output column for each combination of input variables determined in the evaluation.

➤ Example:

Inputs				Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	$A(B + CD)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$A = C = D = 1$

$A = B = 1$

Logic Simplification Using Boolean Algebra

- **Goal:** Given a logic circuit, can we construct an **equivalent** circuit with **fewer** number of gates?!
 - “Equivalent” means “has the same Truth Table”.


- **Method:**

1. **Derive** Boolean expression for the logic circuit (i.e., output).
2. **Simplify** Boolean expression (using laws, rules, and theorems).
3. **Construct** logic circuit from the simplified Boolean Expression.

Logic Simplification Using Boolean Algebra

1. Derive Boolean expression for logic circuit.

➤ Example:

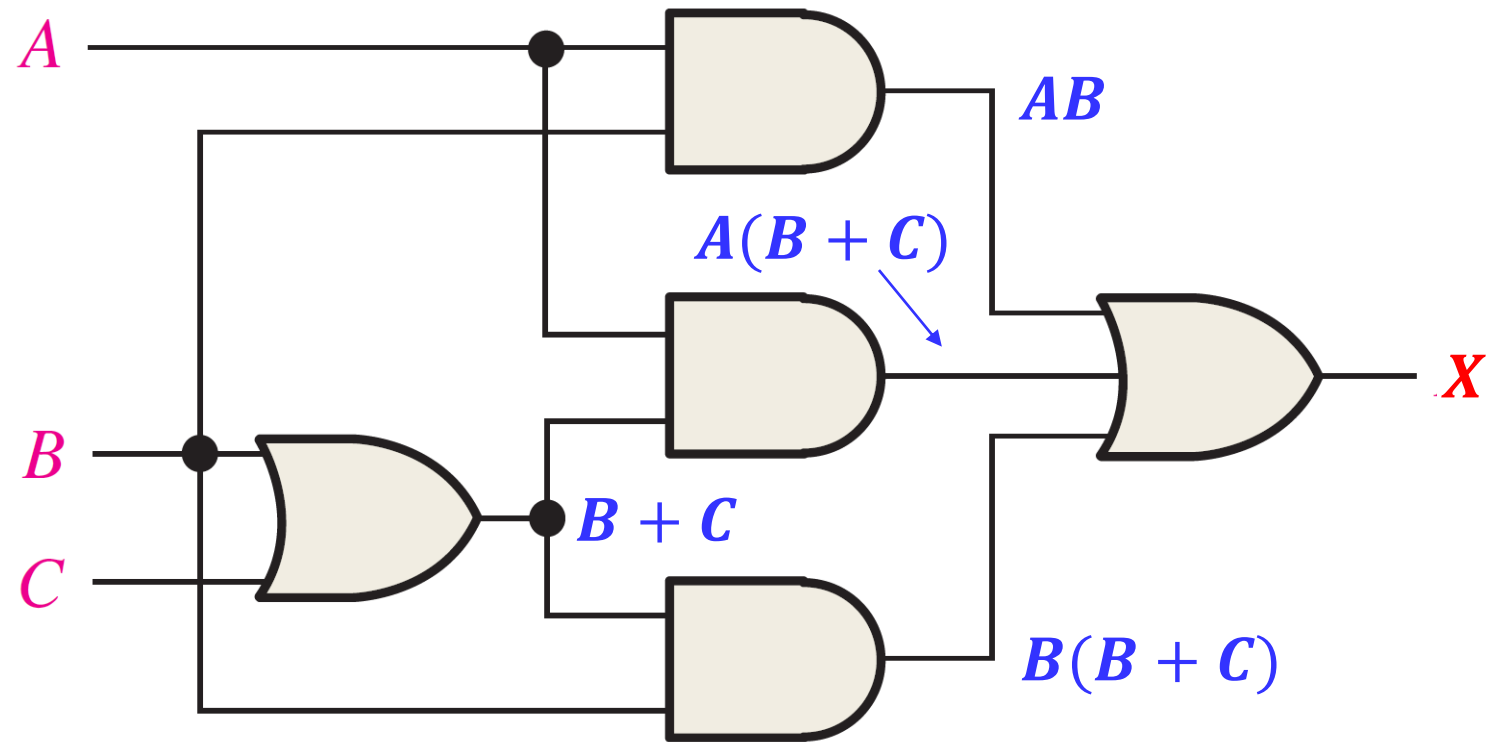

$$X = AB + A(B + C) + B(B + C)$$

Logic Simplification Using Boolean Algebra

2. Simplify Boolean expression.

➤ Example:


- $X = AB + A(B + C) + B(B + C)$ [DL]
- $= AB + AB + AC + BB + BC$ [R7]
- $= AB + AB + AC + B + BC$ [R5]
- $= AB + AC + B + BC$ [R10]
- $= AB + AC + B$ [R10]
- $= B + AC$

Logic Simplification Using Boolean Algebra

3. Construct logic circuit from simplified Boolean Expression

➤ Example:

$$X = B + AC$$

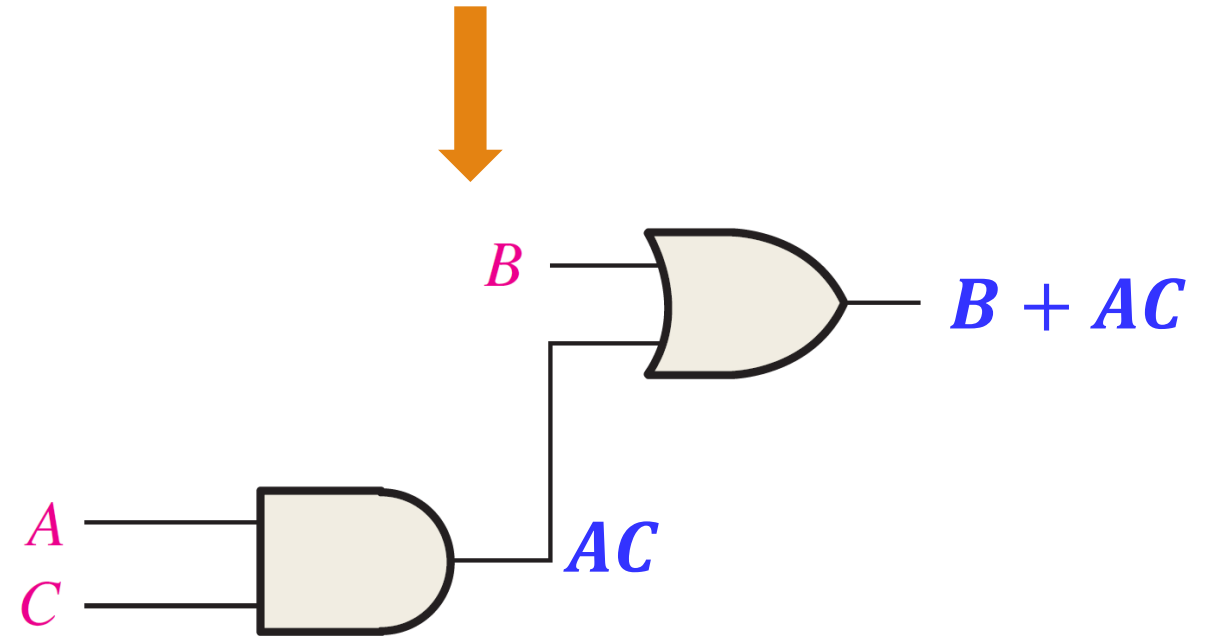

Standard Forms of Boolean Expressions

➤ All Boolean expressions, regardless of their form, can be converted into either of two standard forms:

1. **Sum-of-products (SOP):** 2^+ product terms added together.

- **Examples:** " $\bar{A}B + A\bar{B}C + \bar{C}$ " and " $\bar{A}\bar{B}\bar{C}\bar{D} + AC + \bar{C}D$ ".
- **Note:** $\bar{A}\bar{B}\bar{C}\bar{D} + AC$ is **not in SOP** form, because first term is not product term!!

2. **Product-of-sums (POS):** 2^+ sum terms multiplied together.


- **Examples:** " $(\bar{A} + B + C)(A + C)$ " and " $(\bar{A} + \bar{B} + \bar{C} + D)(\bar{B} + C)(A + D)$ ".
- **Note:** $(\bar{A} + \bar{B} + \bar{C} + D)(\bar{B} + C)$ is **not in POS** form, because first term is not sum term!!

Implementing SOP & POS Expressions

IMPLEMENTING SOP EXPRESSIONS

➤ **ORing** outputs of 2+ **AND** gates


➤ **Example:**

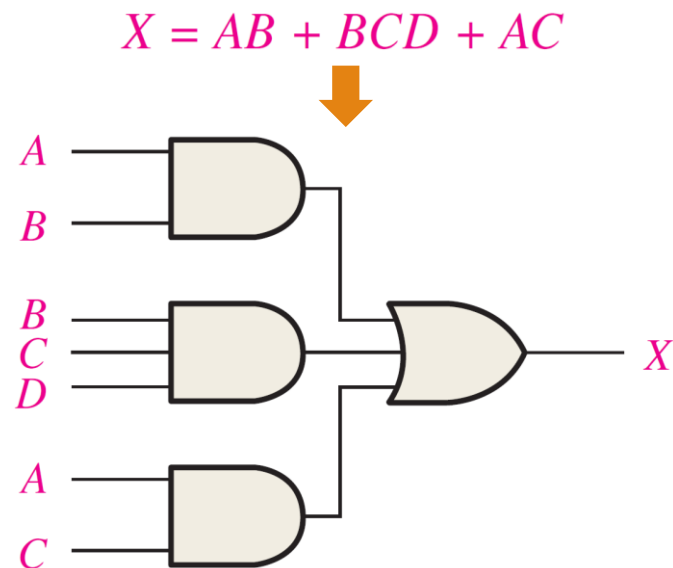

IMPLEMENTING POS EXPRESSIONS

➤ **ANDing** outputs of 2+ **OR** gates

➤ **Example:**

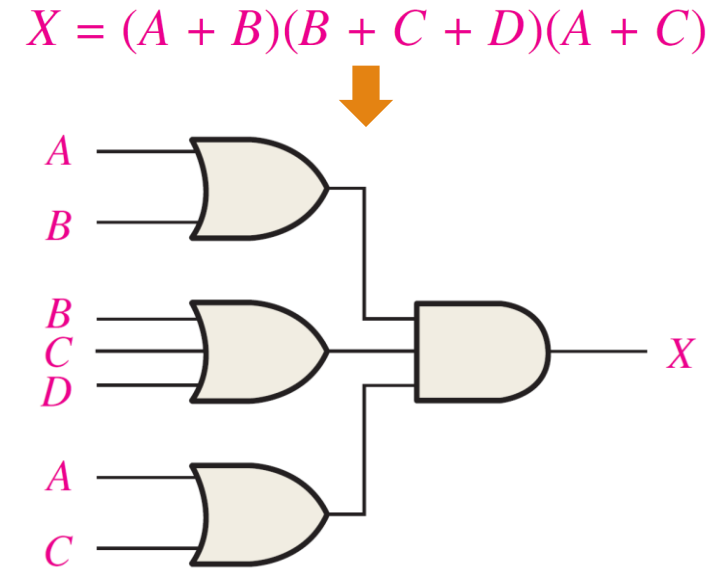

Standard SOP & POS Expression

STANDARD SOP EXPRESSION

➤ Every **product term** must contain all variables!

➤ **Example:**

- Non-standard SOP
 - $A\bar{B} + \bar{A}BC$
 - “**C**” is missing in 1st term!
- Standard SOP
 - $A\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC$

STANDARD POS EXPRESSION

➤ Every **sum term** must contain all variables!

➤ **Example:**

- Non-standard POS
 - $(\bar{A} + C)(A + B + \bar{C})$
 - “**B**” is missing in first term!
- Standard POS
 - $(\bar{A} + \bar{B} + C)(\bar{A} + B + C)(A + B + \bar{C})$

Conversion: General Expression \rightarrow SOP

➤ **Method:** Apply Boolean laws, rules, and theorems!

- Use **DMT** and **R9** to get rid of **term negations**!
- Use **DL** to **distribute a term** over a sum of terms!

➤ **Example:** Convert $\overline{(\overline{A + B}) + C}$ to SOP form.

➤ **Solution:**

- $\overline{(\overline{A + B}) + C} = (\overline{\overline{A + B}})\overline{C}$ [DMT]
- $= (A + B)\overline{C}$ [R9]
- $= A\overline{C} + B\overline{C}$ [DL]

Conversion: SOP \rightarrow Standard SOP

➤ **Method:** For each product term that misses a variable X , multiply that term by $X + \bar{X}$ (R4 & R6), and then apply DL!

➤ **Example:** Convert to $A\bar{B} + \bar{A}BC$ to standard SOP.

➤ **Solution:**

$$\begin{aligned} \circ A\bar{B} + \bar{A}BC &= A\bar{B}(C + \bar{C}) + \bar{A}BC && \text{[R4 \& R6]} \\ \circ &= A\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC && \text{[DL]} \end{aligned}$$

Conversion: POS \rightarrow Standard POS

- **Method:** For each sum term that misses a variable X , Add $X\bar{X}$ to that term (R1 & R8), and then apply R12!
- **Example:** Convert $(\bar{A} + C)(A + B + \bar{C})$ to standard POS.
- **Solution:**
 - $(\bar{A} + C)(A + B + \bar{C}) = (\bar{A} + C + B\bar{B})(A + B + \bar{C})$ [R4 & R6]
 - $= (\bar{A} + \bar{B} + C)(\bar{A} + B + C)(A + B + \bar{C})$ [R12]

Conversion: Standard SOP → Truth Table

Method: For each product term, determine binary value of inputs that makes it 1, and then place a 1 in output column at corresponding row. Place 0's in all remaining rows.

➤ **Example:** Develop truth table for the standard SOP expression: $\bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$

Inputs			Output	Product Term
A	B	C	X	
0	0	0	0	
0	0	1	1	$\bar{A}\bar{B}C$
0	1	0	0	
0	1	1	0	
1	0	0	1	$A\bar{B}\bar{C}$
1	0	1	0	
1	1	0	0	
1	1	1	1	ABC

Conversion: Standard POS → Truth Table

Method: For each sum term, determine binary value of inputs that makes it 0, and then place a 0 in output column at corresponding row. Place 1's in all remaining rows.

➤ **Example:** Develop truth table for the standard POS expression: $(A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + \bar{C})$

Inputs			Output	Sum Term
A	B	C	X	
0	0	0	0	$(A + B + C)$
0	0	1	1	
0	1	0	0	$(A + \bar{B} + C)$
0	1	1	0	$(A + \bar{B} + \bar{C})$
1	0	0	1	
1	0	1	0	$(\bar{A} + B + \bar{C})$
1	1	0	0	$(\bar{A} + \bar{B} + C)$
1	1	1	1	

Conversion: Truth Table → Standard SOP

Method: Identify binary values of inputs that make output = 1. Convert each binary value to a product term replacing each 1 with corresponding var. and 0 with corresponding var. complement

➤ **Example:** Construct standard SOP expression from following truth table:

Inputs			Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>X</i>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


$X = \bar{A}BC + A\bar{B}\bar{C} + AB\bar{C} + ABC$

Conversion: Truth Table → Standard POS

Method: Identify binary values of inputs that make output = 0. Convert each binary value to a sum term replacing each 0 with corresponding var. and 1 with corresponding var. complement.

➤ **Example:** Construct standard POS expression from following truth table:

Inputs			Output
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

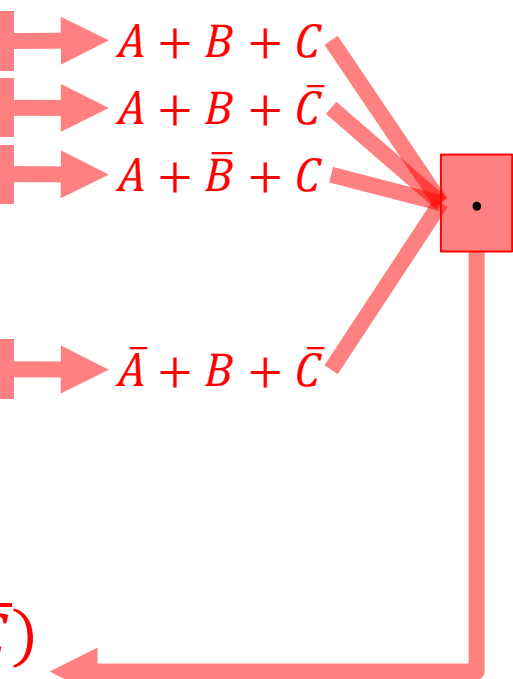

$$X = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(\bar{A} + B + \bar{C})$$

Conversion: Stand. POS \leftrightarrow Stand. SOP

➤ Standard SOP \rightarrow Standard POS:

◦ Method:

1. Standard SOP \rightarrow truth table
2. Truth table \rightarrow standard POS

➤ Standard POS \rightarrow Standard SOP:

◦ Method:

1. Standard POS \rightarrow truth table
2. Truth table \rightarrow standard SOP

Reading Material

- Floyd, Chapter 4:
 - Pages 179 - 199