


* Implement Z using a Mux:

Given:

A	B	C	Z
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Solution:

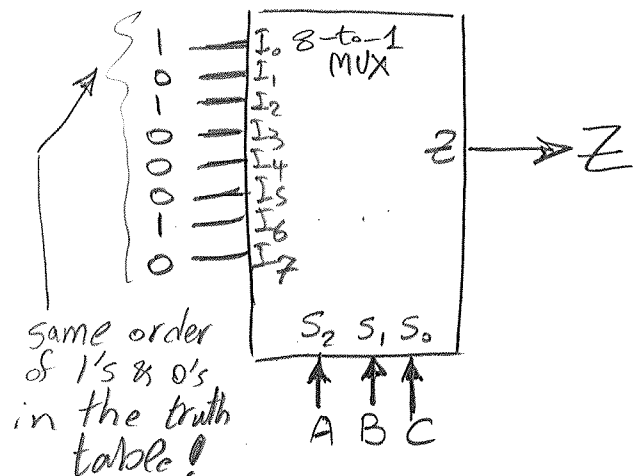Since we have 3 i/p's \Rightarrow
we need to use a Mux with
3 select lines \Rightarrow 8-to-1




Given: $Z = A + \bar{B}$

Solution:



First convert to standard SOP

$$\begin{aligned} Z &= A(B + \bar{B}) + (\bar{A} + A)\bar{B} \\ &= AB + A\bar{B} + \bar{A}\bar{B} + A\bar{B} \\ &= \underbrace{AB}_{I_3} + \underbrace{A\bar{B}}_{I_2} + \underbrace{\bar{A}\bar{B}}_{I_0} \end{aligned}$$

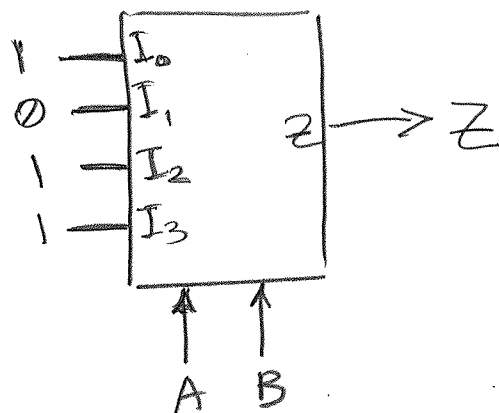Since we have 2 i/p's
 \Rightarrow we need a Mux with 2
select lines \Rightarrow 4-to-1





* Implement a 3-to-8 Decoder using a DEMUX

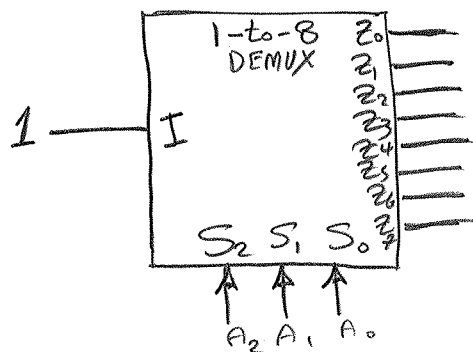
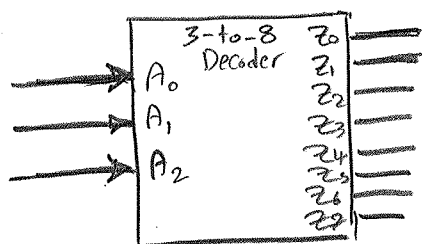


Ch 7:

1

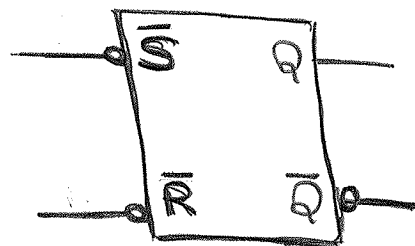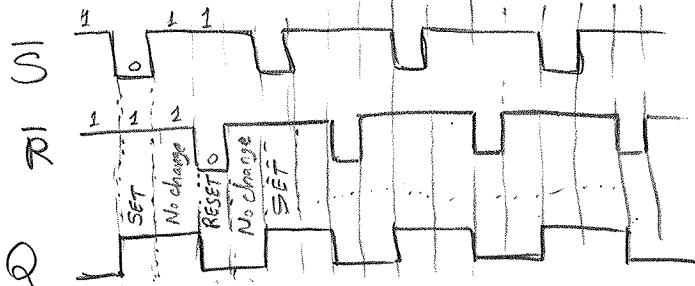

4

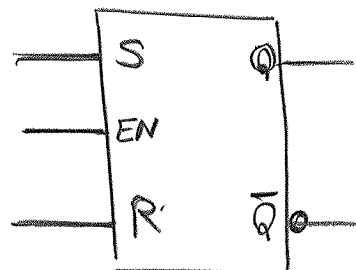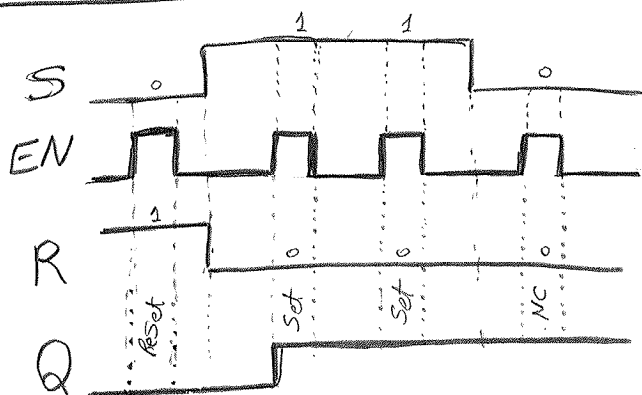

7

