

CSC 211 - Digital Logic Design

211 عال - تصميم المنطق الرقمي

First Term - 1439/1440
Lecture #9

Dr. Hazem Ibrahim Shehata

Assistant Professor

College of Computing and Information Technology

Administrivia

- Assignment #2:
 - To be released on Sunday.

Website: <http://hshehata.github.io/courses/su/cs211>



Chapter 5: Combinational Logic Analysis

Types of Digital Logic Circuits

➤ There are two types of Digital Logic Circuits:

1. Combinational Logic Circuits:

- Output is a pure function in the **present** inputs only!
- **Examples**: adders, subtractors, encoder, decoders, multiplexers, ... etc.

2. Sequential Logic Circuits:

- Output depends not only on the **present** input but also on the **history** of the input!!
- **Examples**: flip-flops, latches, registers, counters, memory, ... etc.

Implementing Combinational Logic

➤ Methods for implementing Combinational Logic:

1. AND-OR Logic

- Usage: implementing SOP and POS expressions

2. NAND Logic

- Usage: implementing SOP expressions

3. NOR Logic


- Usage: implementing POS expressions

4. ...

Implementing SOP expressions using AND-OR Logic

- Each product term is implemented by an AND gate whose inputs are the literals of the product term.
- All the outputs of the AND gates are fed to an OR gate.

 ➤ Example: SOP → AND-OR logic
$$X = \bar{A}BC + A\bar{B}\bar{C}$$




Implementing POS expressions using AND-OR Logic

- Each sum term is implemented by an OR gate whose inputs are the literals of the product term.
- All the outputs of the OR gates are fed to an AND gate.


➤ Example: POS → AND-OR logic
 
$$X = (A + \bar{B})(B + C + D)(\bar{A} + D)$$



Universality of NAND gate

 - NAND gates can be used to implement all other gates: NOT, AND, OR, NOR!!
- Hence, NAND gates can be used to implement any combinational circuit!!!




Implementing SOP expressions using NAND Logic

- Start from the AND-OR implementation (like slide #7) and then replace each:
 - Inverter \rightarrow NAND gate (Connected inputs).
 - AND \rightarrow NAND
 - OR \rightarrow NAND


➤ Example: SOP \rightarrow NAND logic

$$X = \bar{A}BC + A\bar{B}\bar{C}$$

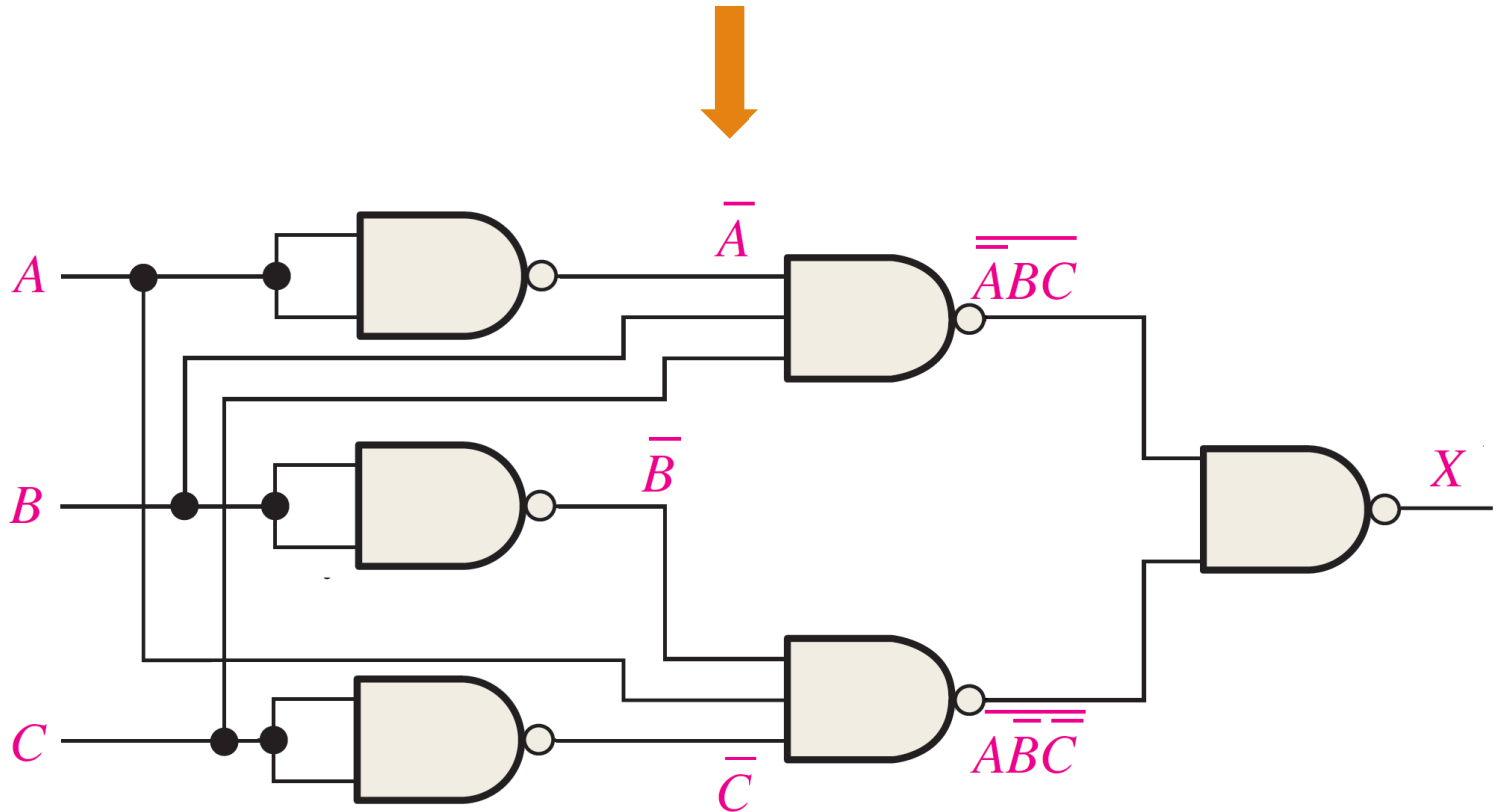

Universality of NOR gate

 - NOR gates can be used to implement all other gates: NOT, AND, OR, NAND!!
- Hence, NOR gates can be used to implement any combinational circuit!!!




Implementing POS expressions using NOR Logic


- Start from the AND-OR implementation (like slide #8) and then replace each:
 - Inverter \rightarrow NOR gate (Connected inputs).
 - OR \rightarrow NOR
 - AND \rightarrow NOR

➤ Example: POS \rightarrow AND-OR logic
 
$$X = (A + \bar{B})(B + C + D)(\bar{A} + D)$$



1

 

2


A	B	$X = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

$\bar{A}B$
 $A\bar{B}$

3


$$X = \bar{A}B + A\bar{B}$$

4

 

Implementing XOR Gate (\oplus) using AND-OR Logic


1

 

2

$$\begin{aligned}
 X &= A \odot B \\
 &= \overline{A \oplus B} \\
 &= \overline{\bar{A}B + A\bar{B}} \\
 &= (A + \bar{B})(\bar{A} + B) \\
 &= A\bar{A} + \bar{A}\bar{B} + AB + B\bar{B} \\
 &= \bar{A}\bar{B} + AB
 \end{aligned}$$

3

 

Implementing XNOR Gate (\odot) using AND-OR Logic



Chapter 6: Functions of Combinational Logic

The Half-Adder

- A **combinational** logic circuit.
- **Purpose:** **adds two bits**, by rules of binary addition:


$$\begin{array}{r} 0 \\ + 0 \\ \hline 0 \end{array}$$


$$\begin{array}{r} 0 \\ + 1 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 1 \\ + 0 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 1 \\ + 1 \\ \hline 10 \end{array}$$

 - **Input/Output:**
 - Accepts **two binary digits**
 - Produces a **sum** bit and a **carry** bit.



 


2

A	B	C_{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

3

$$C_{out} = AB$$

 
$$\Sigma = \bar{A}B + A\bar{B} = A \oplus B$$




Implementing the Half Adder

The Full-Adder

 - A **combinational** logic circuit.
- **Purpose**: adds three bits
- **Input/Output**:
 - Accepts **two binary digits** & **input carry**
 - Produces a **sum** bit and a **carry** bit.



1

 

2

A	B	C _{in}	C _{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


3

$$\begin{aligned}
 C_{out} &= \bar{A}BC_{in} + A\bar{B}C_{in} + AB\bar{C}_{in} + ABC_{in} \\
 &= (\bar{A}B + A\bar{B})C_{in} + AB(\bar{C}_{in} + C_{in}) \\
 &= (A \oplus B)C_{in} + AB
 \end{aligned}$$


$$\begin{aligned}
 \Sigma &= \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in} \\
 &= (\bar{A}\bar{B} + AB)C_{in} + (\bar{A}B + A\bar{B})\bar{C}_{in} \\
 &= (A \odot B)C_{in} + (A \oplus B)\bar{C}_{in} \\
 &= \overline{(A \oplus B)}C_{in} + (A \oplus B)\bar{C}_{in} \\
 &= (A \oplus B) \oplus C_{in}
 \end{aligned}$$

Implementing the Full Adder

3


 


4

 

Implementing the Full Adder

4

  

Implementing the Full Adder

Reading Material

➤ Floyd, Chapter 5:

- Pages 234 – 235, 237, 239 – 248, 250, 252 – 255

➤ Floyd, Chapter 6:

- Pages 285 - 289