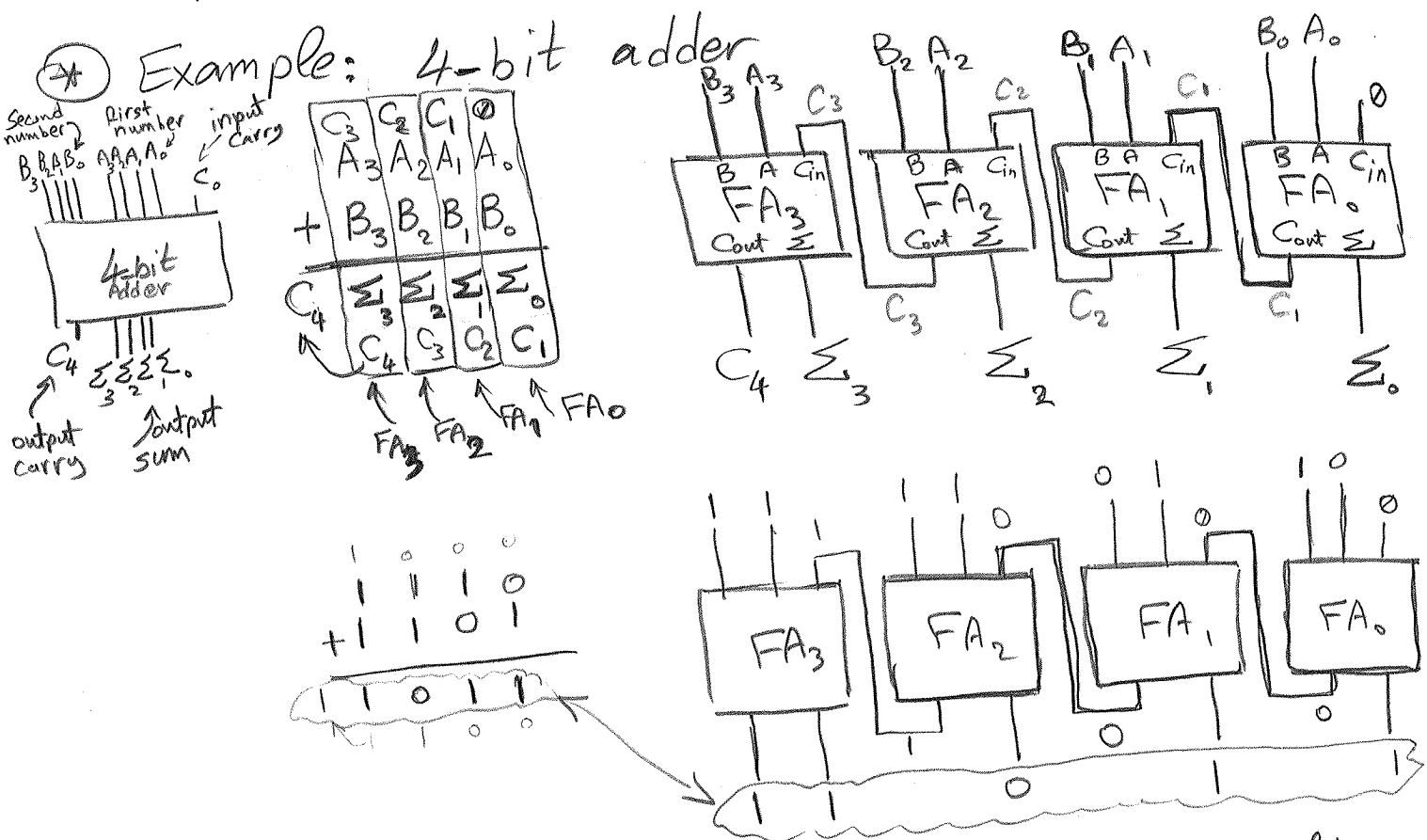



# \* Parallel Binary Adders:

- (\*) To add two binary numbers, a Full-adder (FA) is required for each bit.



- (\*) Adders can be cascaded together to build bigger Adders.

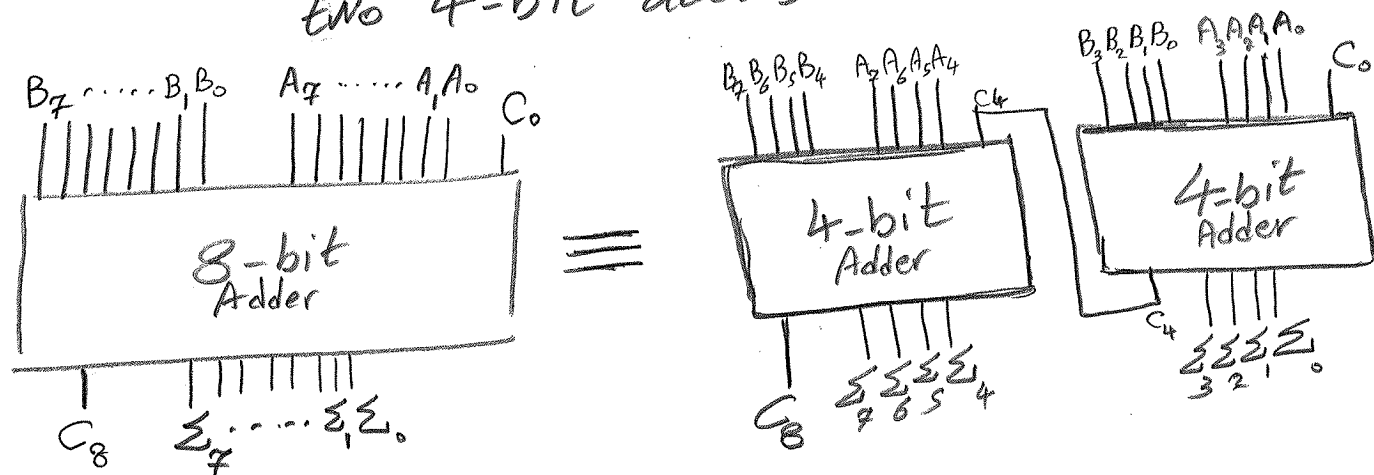- (\*) Example: 8-bit adder can be build from two 4-bit adders as follows:




# \* Comparators :


\* Purpose: Compare two binary numbers A, B for equality :

$$A=B \Rightarrow Z=1$$

$$A \neq B \Rightarrow Z=0$$

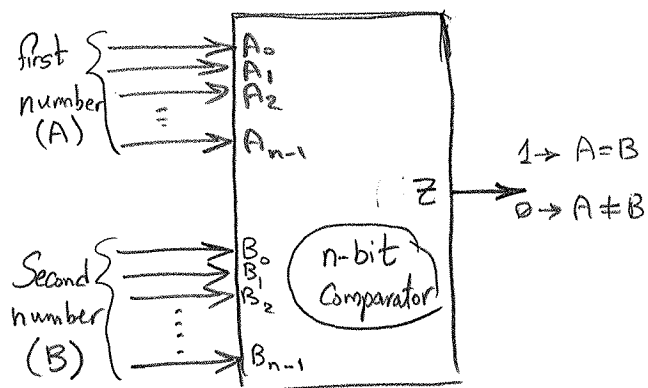


\* Example: 1-bit Comparator

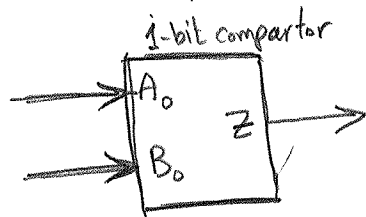


A <sub>0</sub>	B <sub>0</sub>	Z
0	0	1
0	1	0
1	0	0
1	1	1

$$Z = A_0 \odot B_0$$

XNOR

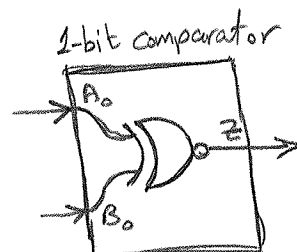

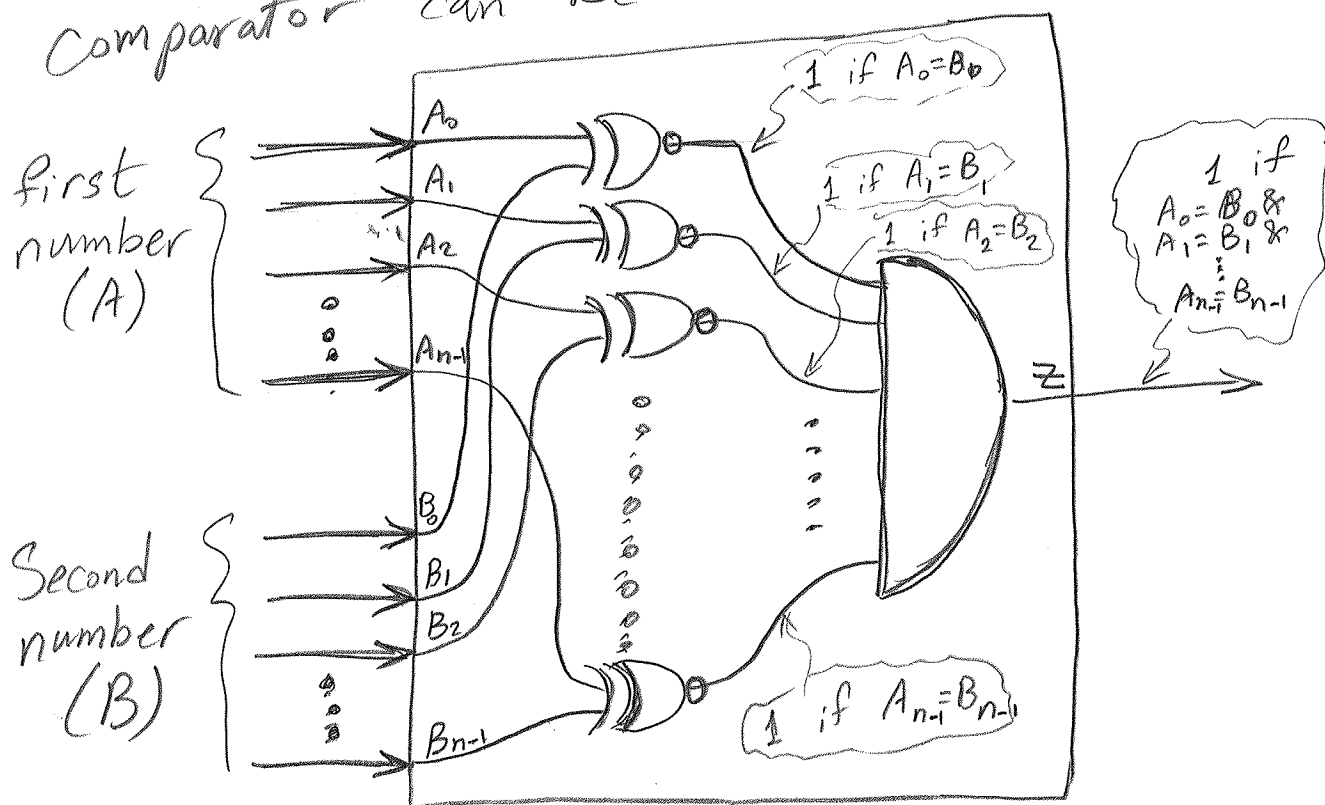\* Since an XNOR gate can be used to compare two single-bit numbers, we need n XNOR gates to compare the corresponding bits of two n-bit numbers. We also need an AND gate with n inputs to combine the results of the n comparisons. So, an n-bit comparator can be constructed as follows:



# \* Decoders:


\* Types: Binary decoders, BCD-to-7-segment decoder, ... etc.

\* Binary decoder: # of inputs # of outputs


\* Commonly called

$n$ -to- $2^n$  decoder

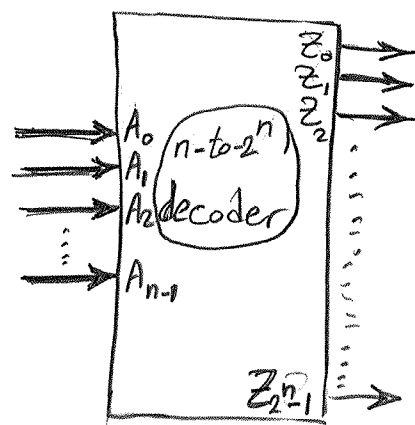
\* purpose: decodes an  $n$ -bit binary number by activating the output which corresponds to the binary number among the  $2^n$  outputs




\* Example: 2-to-4 decoder

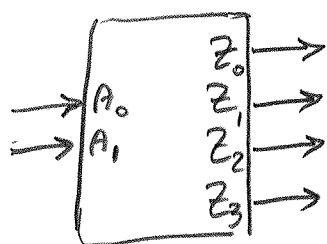

$A_1$	$A_0$	$Z_0$	$Z_1$	$Z_2$	$Z_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

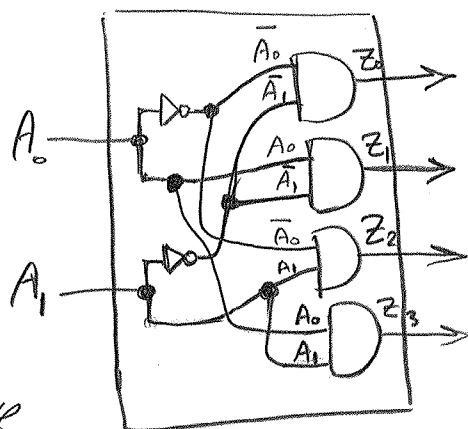

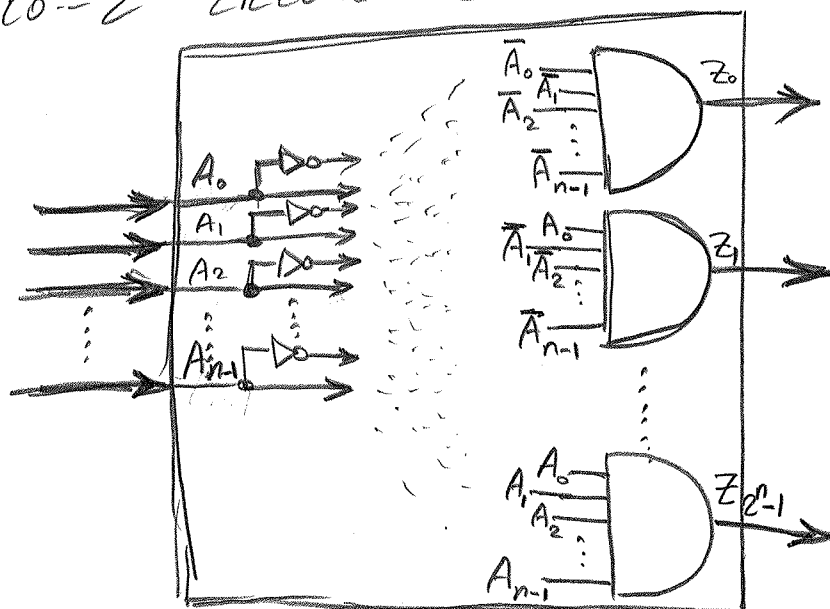\* To build an  $n$ -to- $2^n$  decoder, we need  $2^n$  AND gates, each AND gate must have  $n$  inputs (i.e., fan-in =  $n$ ). So an  $n$ -to- $2^n$  decoder can be constructed as follows:




# \* Encoders:

Types: Binary Encoders, Priority Encoders, .... etc


\* Binary Encoders:

\* Commonly called  $2^n$ -to- $n$  encoders

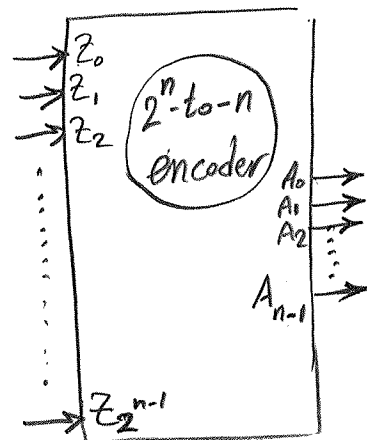
\* purpose: Receives  $2^n$  bits (among which only 1 bit is active, i.e., equals 1) and sets the output to equal the binary value of the position of the active bit.




\* Example: 4-to-2 encoder

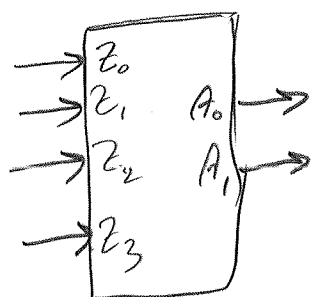


$z_3$	$z_2$	$z_1$	$z_0$	$A_1$	$A_0$
0	0	0	0	X	X
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	X	X
0	1	0	0	1	0
0	1	0	1	X	X
1	0	0	0	1	1
1	0	0	1	X	X

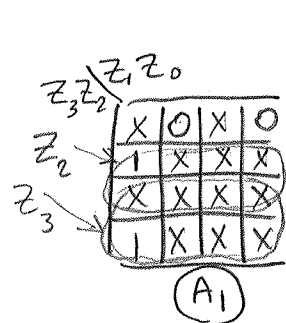

$$A_1 = z_2 + z_3$$

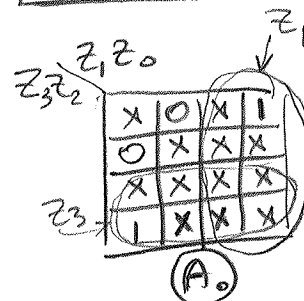

$$A_0 = z_1 + z_3$$

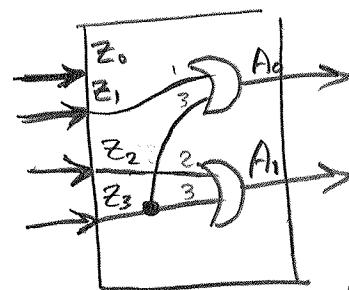

\* To build a  $2^n$ -to- $n$  encoder, we need

$n$  OR gates

Notes:  $A_0 = 1$  when position equals:

- 1  $\rightarrow$  00...001
- or 3  $\rightarrow$  00...011
- or 5  $\rightarrow$  00...101
- or 7  $\rightarrow$  00...111

