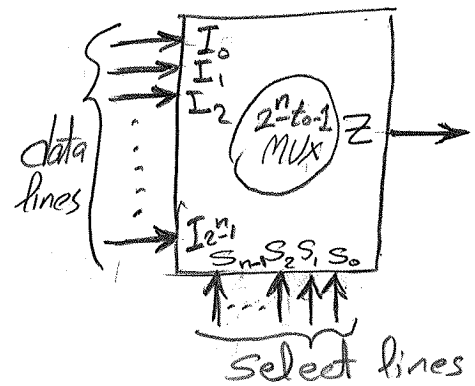



* Multiplexers: (Data Selectors)

* Commonly called 2^n -to-1 MUX


* purpose: Receives 2^n bits of data and an n -bit binary code and selects the data bit whose position is determined by the code (on the select lines), and passes it along to the output Z .




* Example: 4-to-1 Mux

 
 
$$Z = I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0$$



 
* To build a 2^n -to-1 Mux, we need 2^n AND gates (each one has $n+1$ inputs) and 1 OR gate with 2^n inputs




* Demultiplexers:

* Commonly called 1-to- 2^n DEMUX

 * purpose: Receives 1 bit of data and an n -bit binary code, and directs the data to the output whose position equals the code (located on the select lines)




* Example: 1-to-4 DEMUX

 


I	S ₁	S ₀	Z ₀	Z ₁	Z ₂	Z ₃
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

$$Z_0 = I \bar{S}_1 \bar{S}_0, \quad Z_1 = I \bar{S}_1 S_0$$
 
$$Z_2 = I S_1 \bar{S}_0, \quad Z_3 = I S_1 S_0$$



 * To build a 1-to- 2^n DEMUX, we need 2^n AND gates (each one has $n+1$ inputs).



Sequential Logic: (Latches, Flip-flops,etc.)

1 Latches:

* A latch is a temporary storage device that has two logic states \rightarrow bistable


* Types: ① **S-R (SET-RESET) Latch** $\begin{cases} \text{Active-high} \\ \text{Active-low} \end{cases}$

② Gated S-R Latch


③ Gated D Latch

① S-R (SET-RESET) Latch

Active High


 


Active Low

 

Logic
Symbol

Logic
Circuit

  



Truth
Table

S	R	Q	Q̄	
0	0	NC	NC	No Change
0	1	0	1	Latch RESET
1	0	1	0	Latch SET
1	1	0	0	Invalid Condition (Should be avoided!!)

Latch remains in present state as Q don't change

S̄	R̄	Q	Q̄	
0	0	1	1	Invalid Condition
0	1	1	0	Latch SET
1	0	0	1	Latch RESET
1	1	NC	NC	No Change

Timing
Diagram

  


Assuming initially Q=0


② Gated S-R Latch

* Logic symbol *

Enable Signal

 

* Logic circuit *

 

Active-high Gated S-R Latch

Active-low S-R Latch


We will consider only the active-high version which is built using an active-low SR Latch

* Truth Table *


EN	S	R	Q	Q̄	
0	0	0	NC	NC	No change
0	0	1	NC	NC	
0	1	0	NC	NC	
0	1	1	NC	NC	
1	0	0	NC	NC	No change
1	0	1	0	1	RESET
1	1	0	1	0	SET
1	1	1	0	0	Invalid

③ Gated D Latch

* Logic Symbol *

 

* Logic Circuit *

 

D-Latch

Gated S-R Latch

* Truth Table *

EN	D	Q	Q̄	
0	0	NC	NC	No Change
0	1	NC	NC	
1	0	0	1	RESET
1	1	1	0	SET

* Timing Diagram *

