

Midterm #2

General Information

- Date: Sunday, December 2nd, 2018
- Duration: 60 minutes
- Total marks: 20

Instructions and Guidelines

- No books or notes are permitted.
- Computer usage is prohibited.
- Cell phones must be turned off.
- Calculators are not allowed.
- Try to answer all questions.
- Write down your answers neatly in this booklet.
- To earn partial marks, justify your answers.
- If you need extra paper, request some from a proctor.

Grading

Question	Q1	Q2	Q3	Q4	Q5	Total
Points	$\overline{4}$	$\overline{3}$	$\overline{5}$	$\overline{3}$	$\overline{5}$	$\overline{20}$

Student Name:

ID Number:


Q1**[4 Points]**

Simplify the following expression using Boolean algebra. Justify each step in your solution by referring to the Boolean rule or law or theorem you use.

$$Z = (B + \bar{B}C)(\overline{A\bar{B}}) + AC + \bar{B}\bar{C}$$

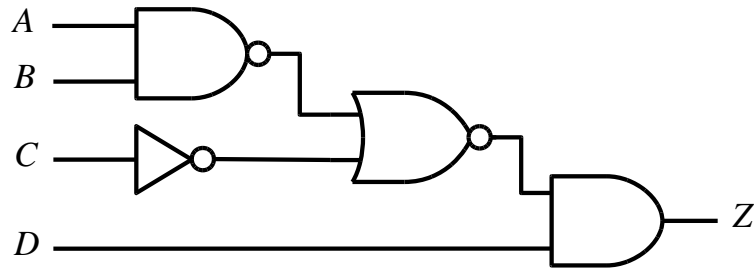Q2**[3 Points]**

Write a Boolean expression for the output of the following circuit (Z) and then simplify that expression using Boolean algebra.



Q3**[5 Points]**

Given below two copies of a Karnaugh map that describes a Boolean variable Z .

a. Construct a minimum SOP expression for Z .

$AB \backslash CD$	00	01	11	10
	00	01	11	10
00	0	X	0	0
01	X	1	1	0
11	X	1	1	1
10	1	0	1	1

b. Construct a minimum POS expression for Z .

$AB \backslash CD$	00	01	11	10
	00	01	11	10
00	0	X	0	0
01	X	1	1	0
11	X	1	1	1
10	1	0	1	1


Q4**[3 Points]**

Implement the following Boolean expression using NOR gates: $Z = A(\bar{B} + C)$.

Q5

[5 Points]

Given the following logic circuit:

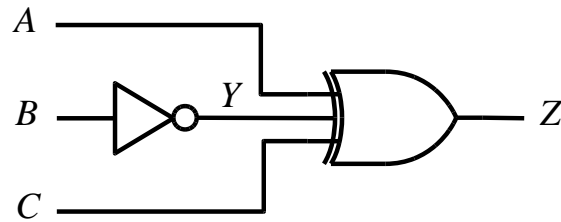

a. Fill up the truth table of Y and Z .

Inputs			Outputs	
A	B	C	Y	Z

b. Draw the waveforms of Y and Z .

