

1. Simplify the following expressions using Boolean algebra:



- $(B + \bar{C})(\bar{B} + C) + \overline{\bar{A} + B + \bar{C}}$
- $\overline{(\bar{A} + B + \bar{C})(A + B + \bar{C})(\bar{A} + B + C)(BC + \bar{A}\bar{B}\bar{C})}$

2. Suppose a Boolean variable Z is described by the following Karnaugh map:

AB \ CD	CD			
	00	01	11	10
00	X	X	X	0
01	0	X	1	1
11	0	1	1	X
10	0	X	X	0

- Construct a minimum SOP expression for Z.
- Construct a minimum POS expression for Z.
- Implement Z using NAND gates.
- Implement Z using NOR gates.

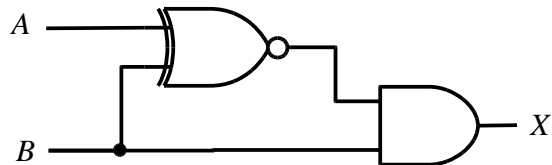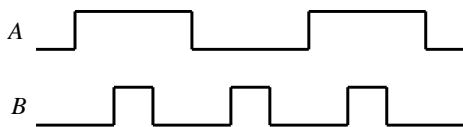3. For the following logic circuit, draw the output waveform in proper relationship to the inputs.



4. Design a logic circuit whose output Z is HIGH only when a majority of its inputs A, B, and C are LOW.